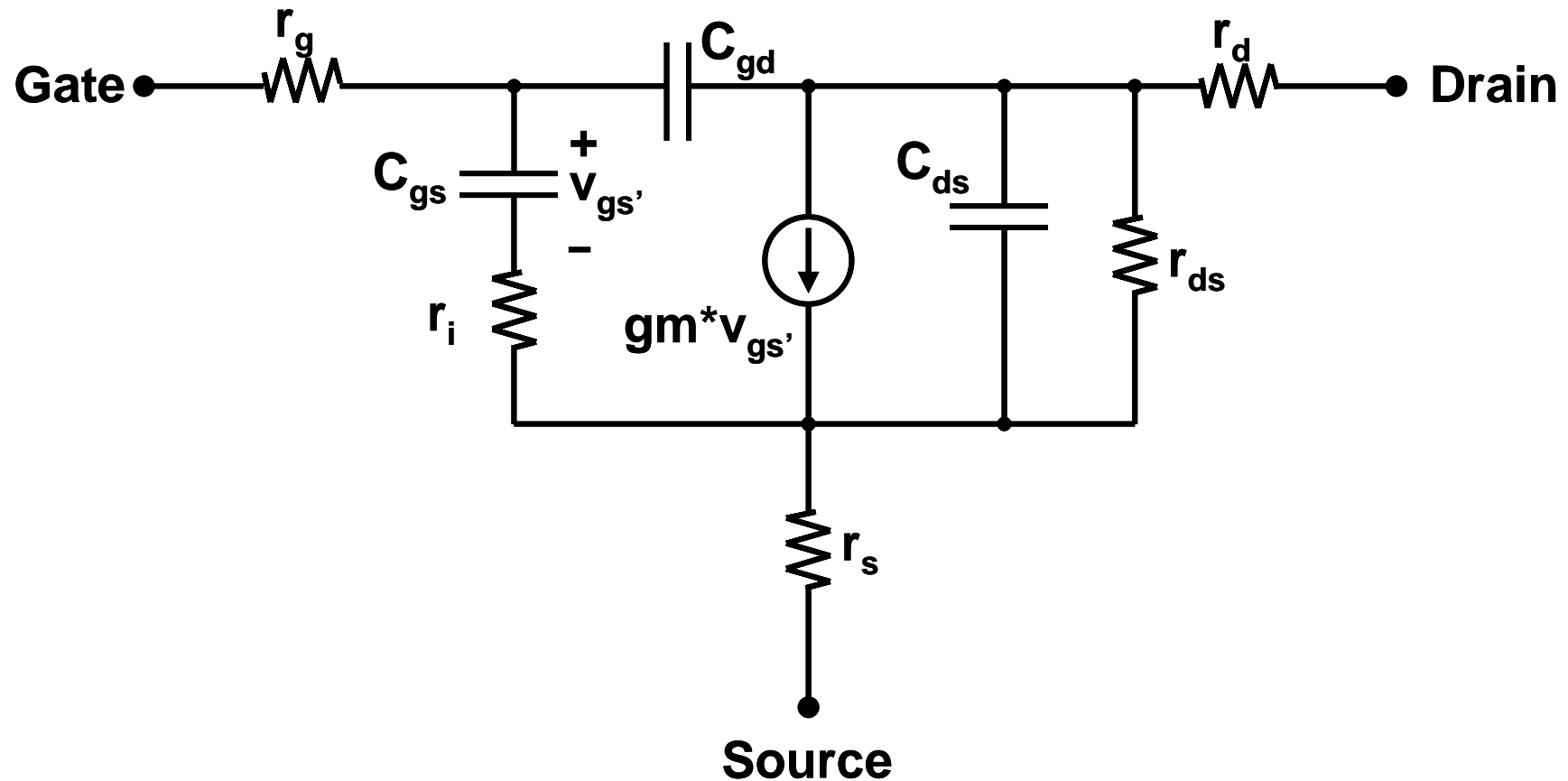


General CMOS small signal circuit



Typically, all capacitances are voltage dependent (function of V_{ds}/V_{gs}), and r_d/r_s are not that small