



**Nokia Siemens
Networks**

Experiences with driver schedules


Eckhard Lenski

DATE , Nice , France


19th April 2007

Agenda


Summary

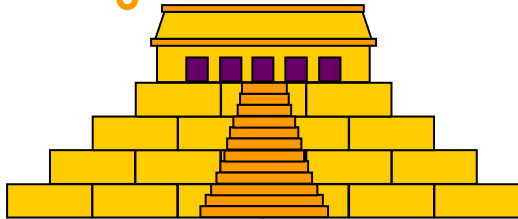


*Experiences with
driver schedules*

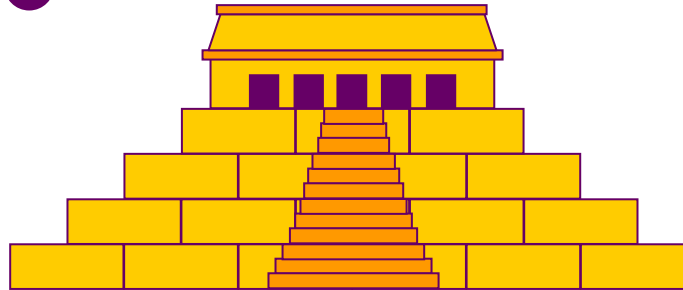


Driver schedules basics

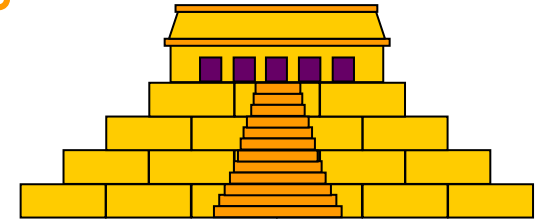


CML- Pre-emphasis

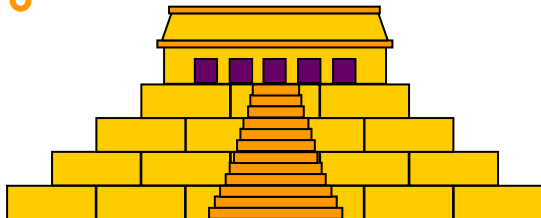


GTL-like

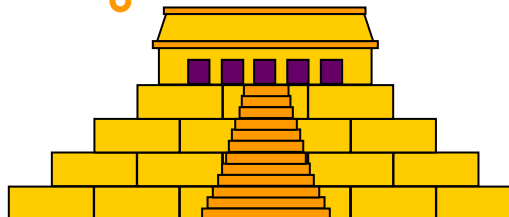

Push-pull

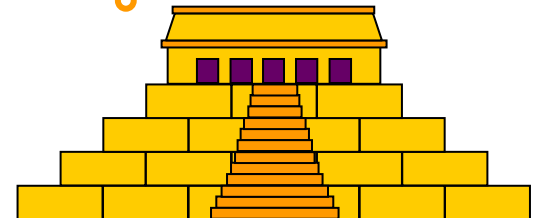



*Driver schedules
basics*

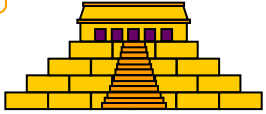

Driver schedule basics...



Multistage driver

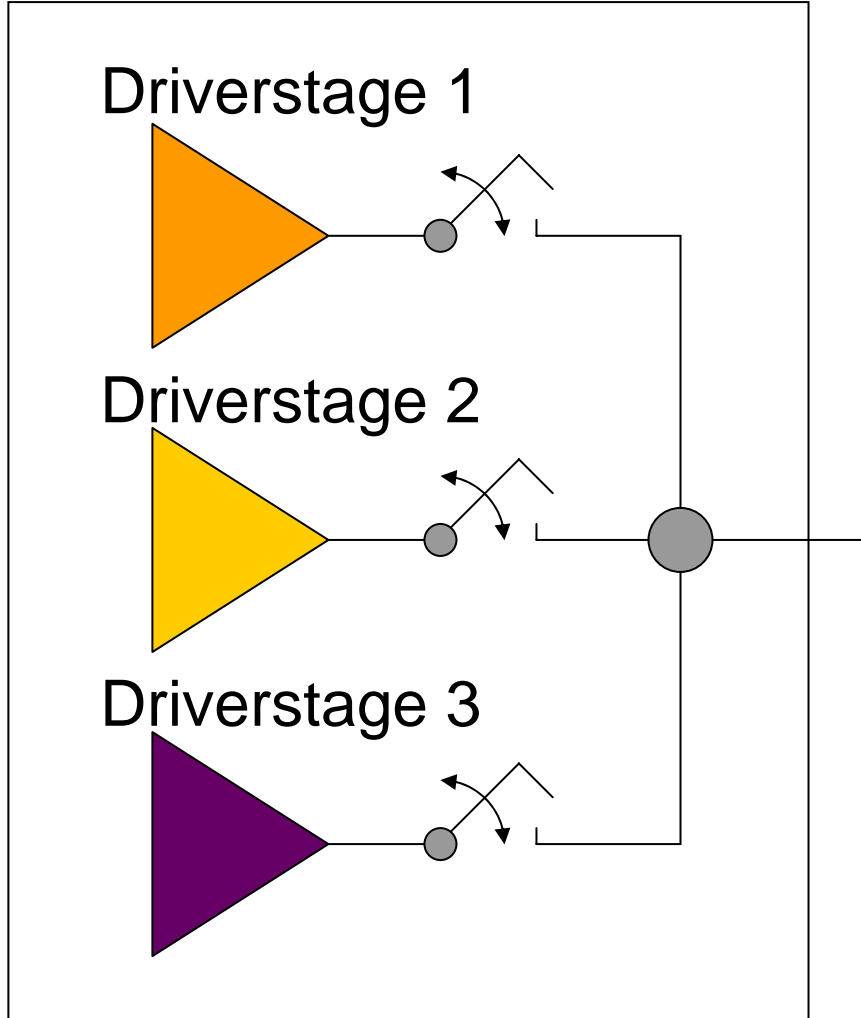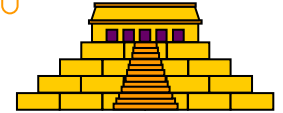

A Multistage driver consists of several driverstages, which are switching at different times

Or different voltage levels

Or

parts of IBIS Multistage driver model

[Model] 3-Driver-schedule

Model_type I/O

Vinl = 0.68V

Vinh = 0.88V

C_comp	1.5pF	1.0pF	2.0pF
--------	-------	-------	-------

[Voltage Range]	3.30V	3.1350V	3.4650V
-----------------	-------	---------	---------

[Driver Schedule]

[Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
-------------	-------------	--------------	-------------	--------------

MODEL_1	0s	NA	0ns	NA
---------	----	----	-----	----

MODEL_2	0.5ns	NA	0ns	NA
---------	-------	----	-----	----

MODEL_3	1.0ns	2.5ns	NA	NA
---------	-------	-------	----	----

[GND Clamp]

[POWER Clamp]

[Pulldown]

[Pullup]

3.00	0.00	0.00	0.00
------	------	------	------

[Ramp]

dV/dt_r	1.00V/1.8ns	0.9V/2.50ns	1.1V/1.0ns
---------	-------------	-------------	------------

dV/dt_f	1.3V/1.5ns	1.1V/2.0ns	1.4V/0.9ns
---------	------------	------------	------------



Parameters

scheduled models

Top level model tables

top level model



C_comp

[Voltage Range] 3.30V

[GND Clamp]

[POWER Clamp]

[Pulldown]

[Pullup]

[Ramp]

dV/dt_r 1.00V/1.8ns


dV/dt_f 1.3V/1.5ns

Top level model tables

For tools, which don't understand the [Driver schedule] keyword, there is a description of the rough/approximate behavior of the output with normal IBIS keywords, (called top level model)



scheduled models

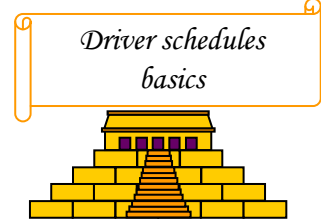

[Model] 3-Driver-schedule

Model_type I/O

[Driver Schedule]

[Model_name]	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
--------------	-------------	--------------	-------------	--------------

MODEL_1	0s	NA	0ns	NA
---------	----	----	-----	----

MODEL_2	0.5ns	NA	0ns	NA
---------	-------	----	-----	----


MODEL_3	1.0ns	2.5ns	NA	NA
---------	-------	-------	----	----

scheduled models

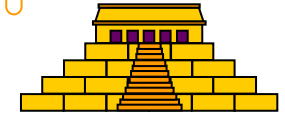The Driver schedule contains the exact timing information about the time, when the different driverstages are used.





The switching behavior of each driverstage itself is described like that of a normal IBIS IO-model in a [Model] statement

scheduled models timing




rising edge (L->H)

falling edge (H->L)


Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
MODEL_1	1.0ns	2.5ns	0ns	NA
				
	turn on pullup- structure	turn off pullup- structure	turn on pulldown- structure	turn off pulldown- structure
	turn off pulldown- structure	turn on pulldown- structure	turn off pullup- structure	turn on pullup- structure

example timing schedule

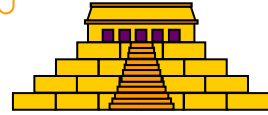


[Driver Schedule]


Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
MODEL_1	0.5ns	NA	0ns	NA
MODEL_2	1.0ns	NA	0ns	NA
MODEL_3	1.5ns	2.5ns	NA	NA

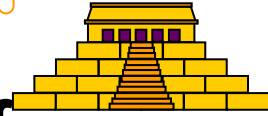


All 3 driver stages are switched off

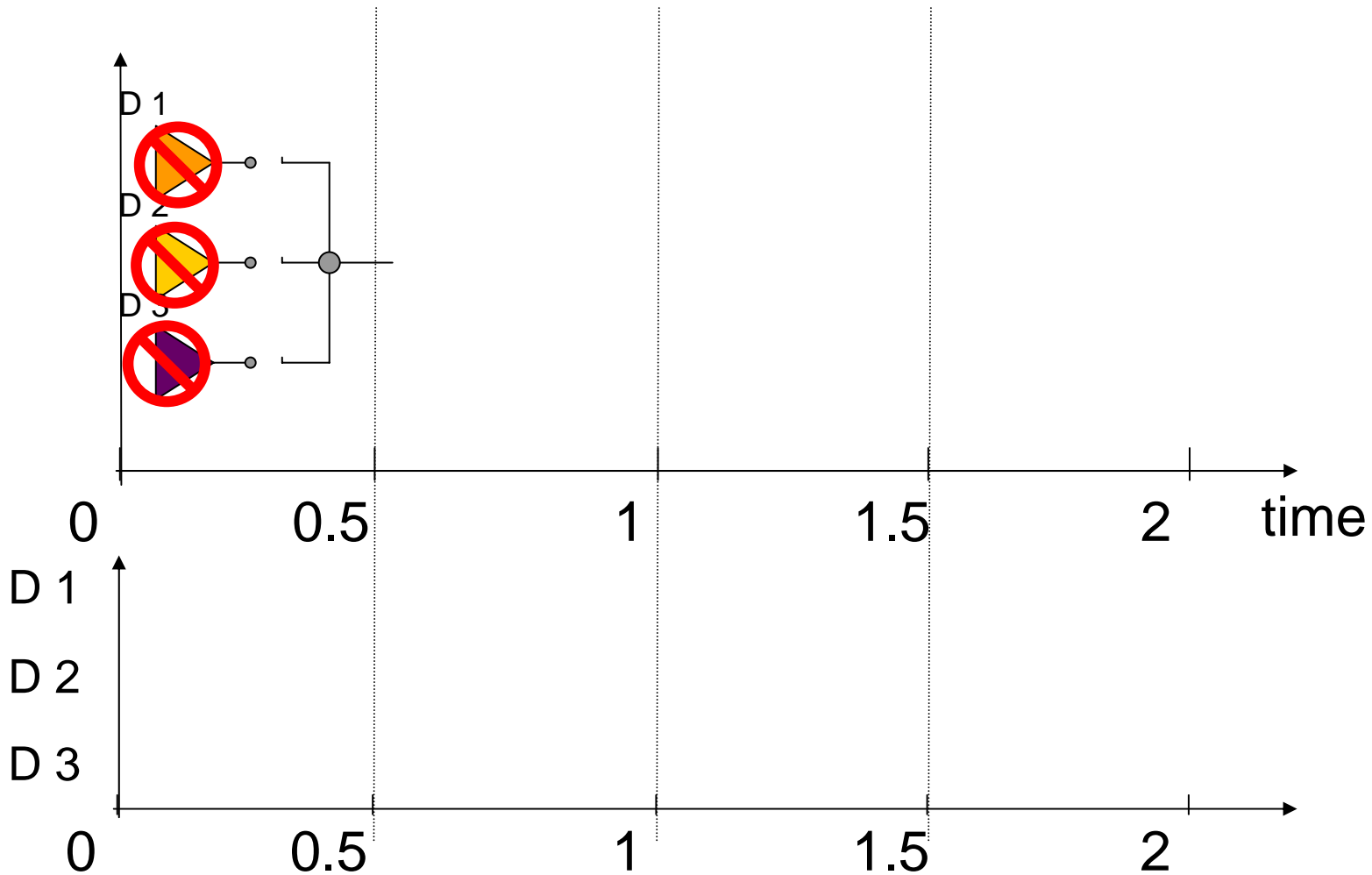


time schedule $t = 0.5$

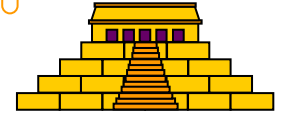


Driver stage D1 is switched on

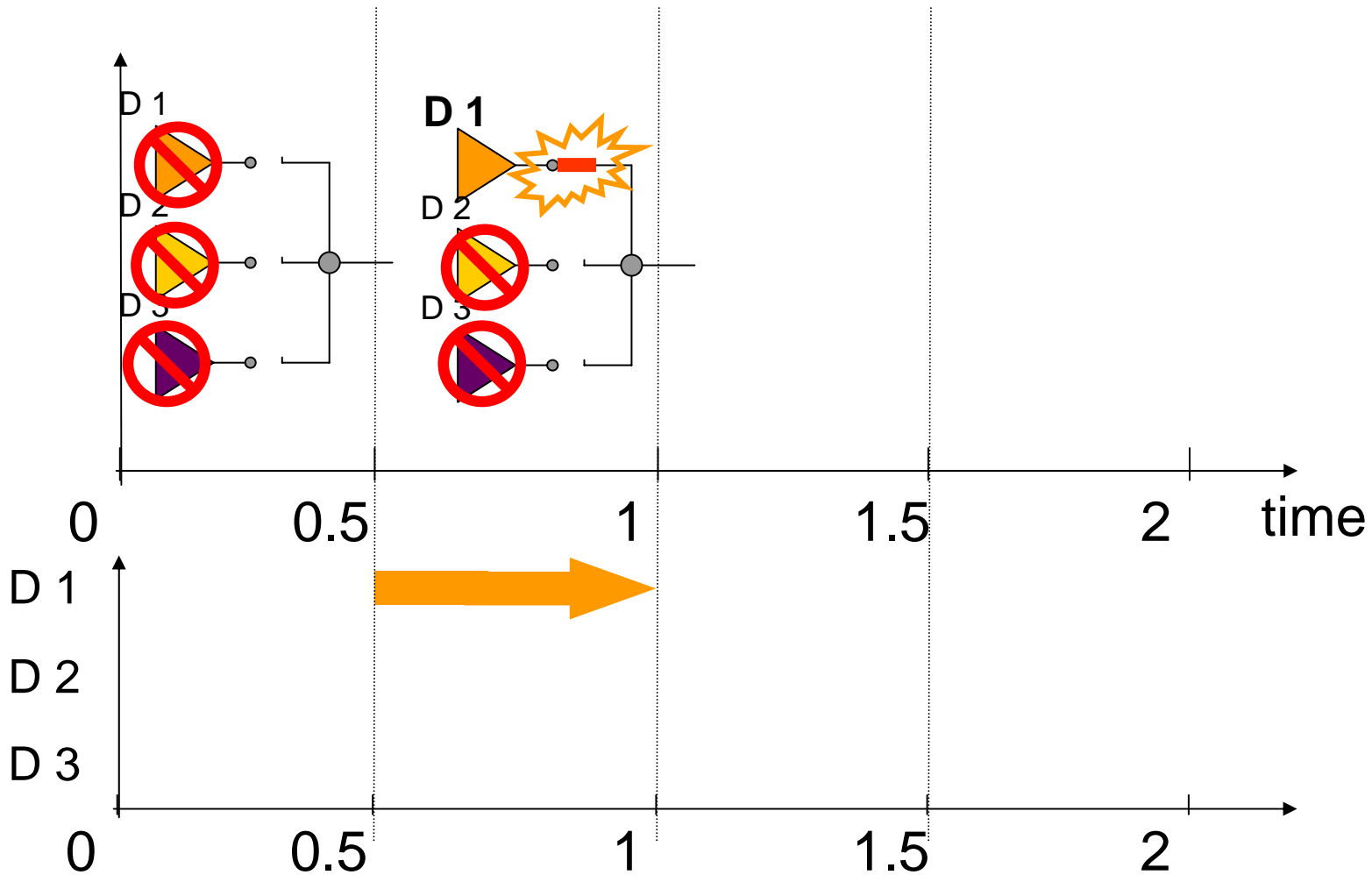

time schedule $t = 1$

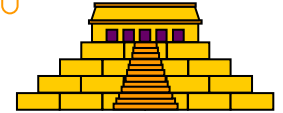

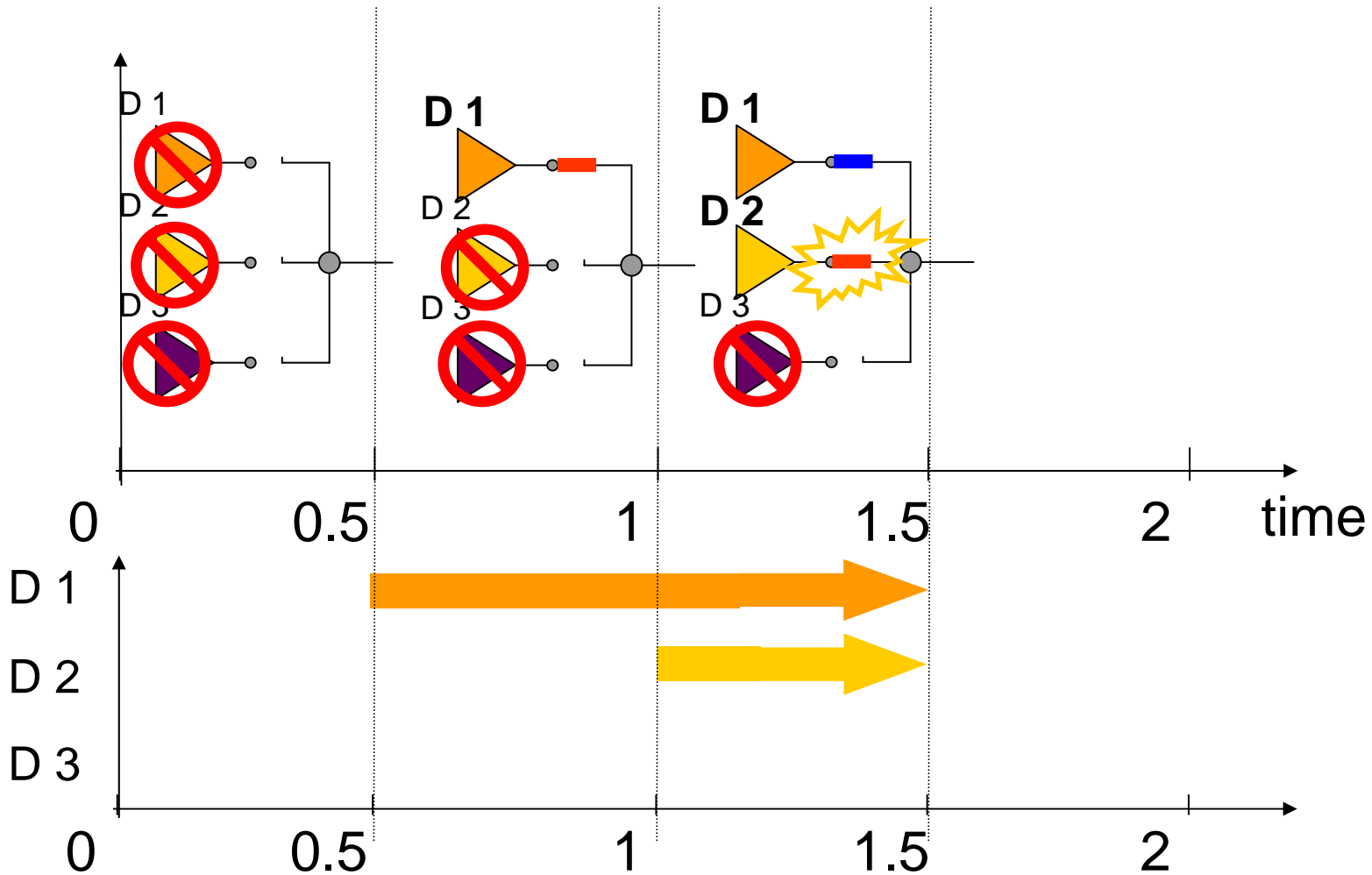Driver stage D2 is additionally switched on




time schedule $t = 1.5$


Driver schedules
basics



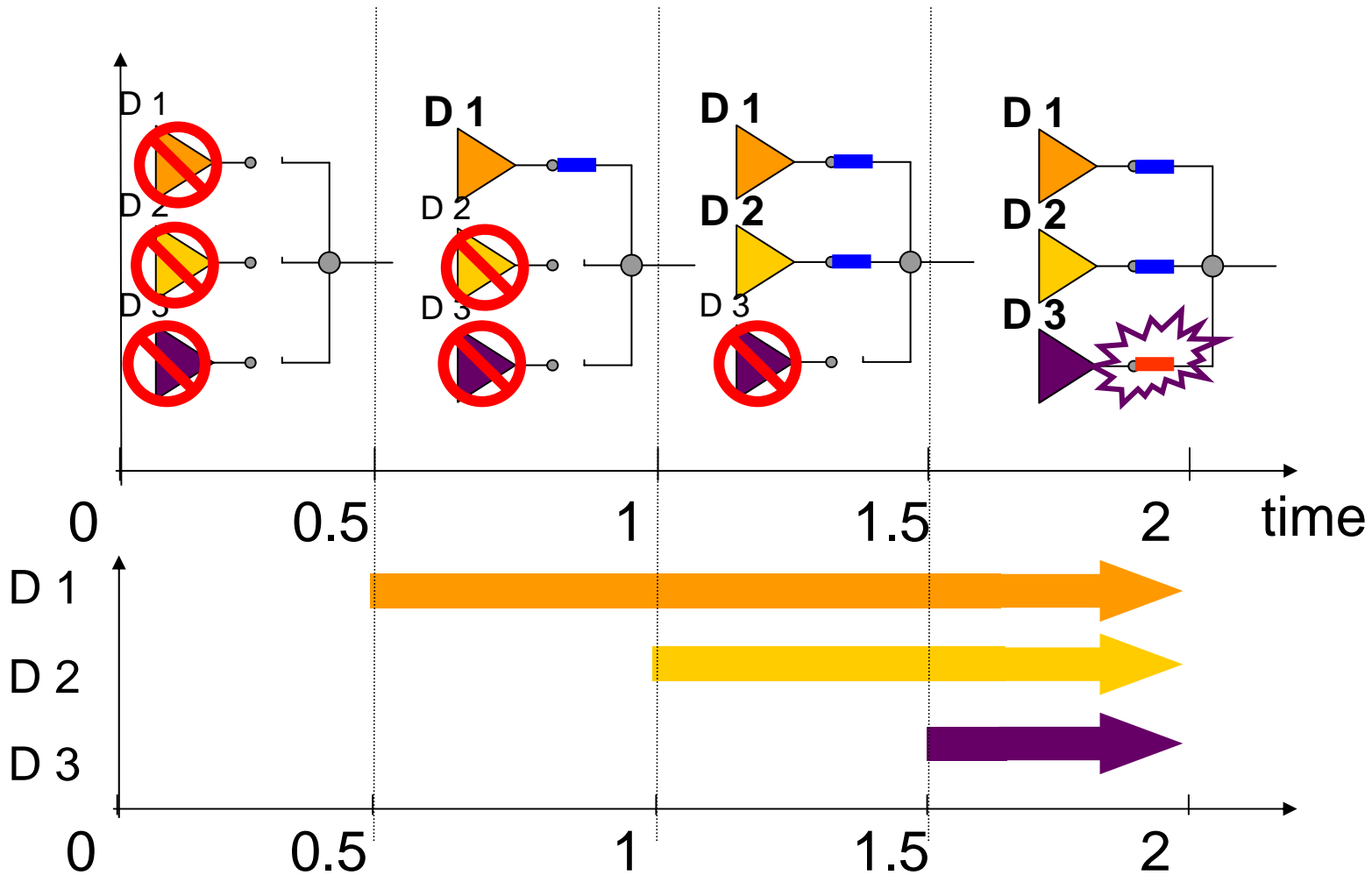
Driver stage D3 is additionally switched on



time schedule $t = 2.5$

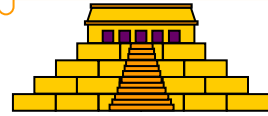

Driver stage D3 is switched off

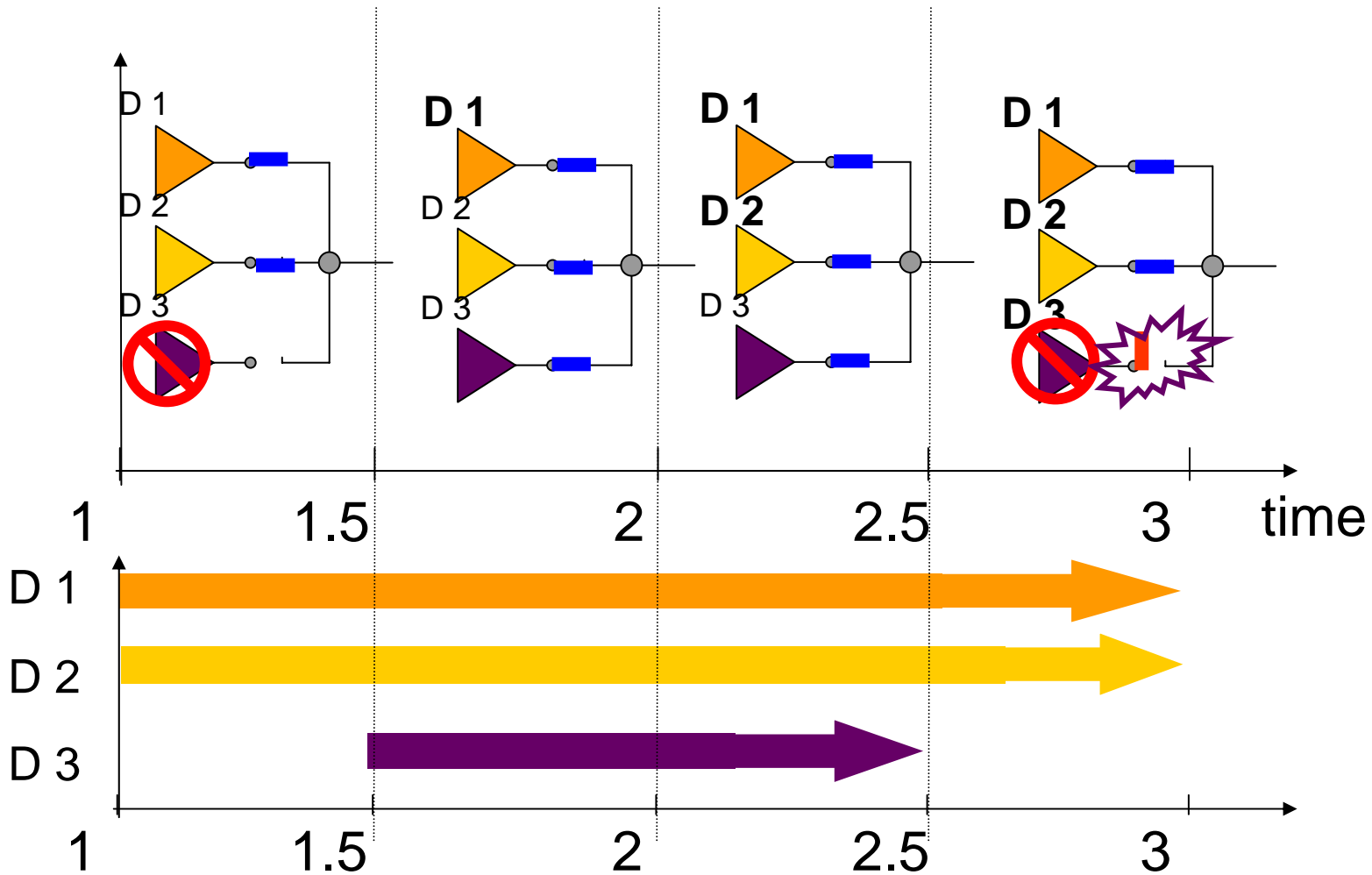


Driver schedules with push-pull (CMOS) Models

Push-pull







IBIS push pull driver schedule




Push-pull

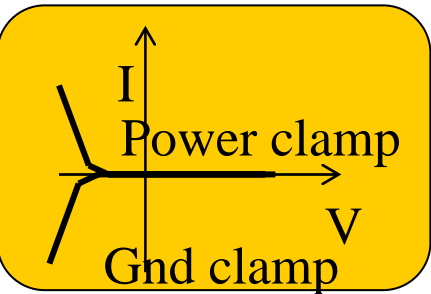

MODEL_1

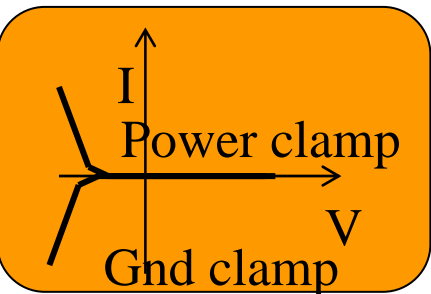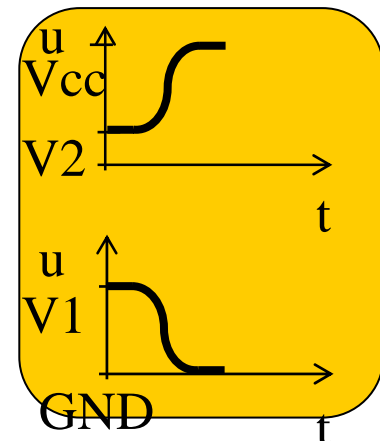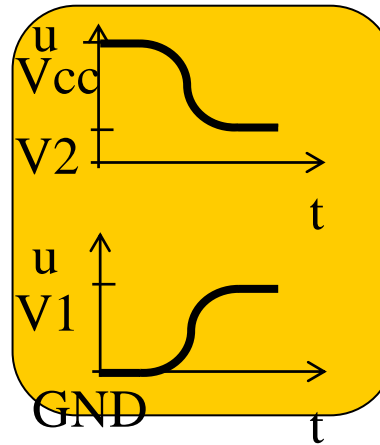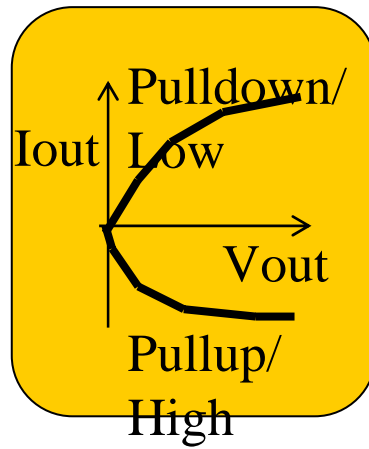

MODEL_2

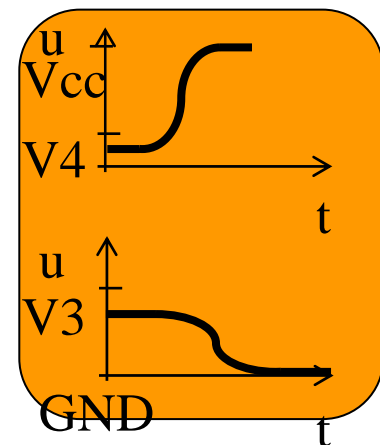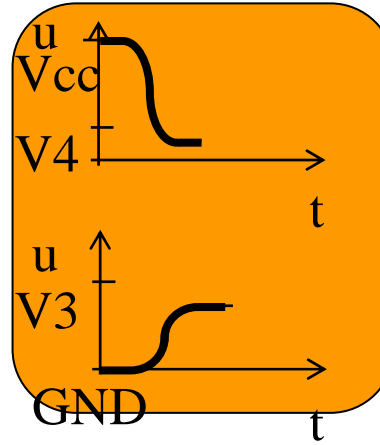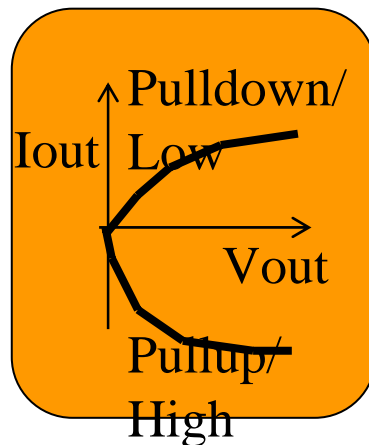



Example with two IO-Models and no top level model information

.....

[Driver schedule]

Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
MODEL_1	2.00ns	NA	2.0ns	NA
MODEL_2	2.50ns	NA	2.0ns	NA


.....

IO-models stand alone


Push-pull



MODEL_1 stand alone

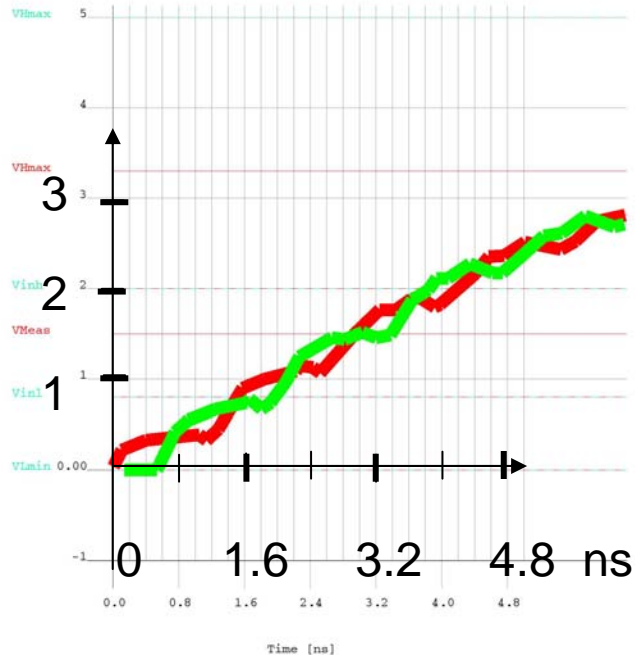

MODEL_2 stand alone

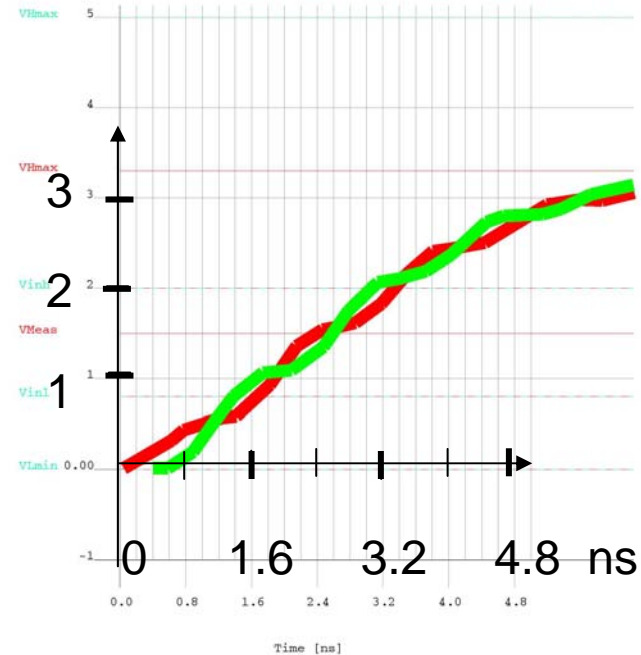

Testload was a 3 inch transmission line (open)

Driver



End of line





3 test cases

(examples show only rising edge)

1

Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
MODEL_1	0.00ns	NA	2.0ns	NA
MODEL_2	0.00ns	NA	2.0ns	NA

2

Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
MODEL_1	0.00ns	NA	2.0ns	NA
MODEL_2	2.50ns	NA	2.0ns	NA

3

Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
MODEL_1	2.00ns	NA	2.0ns	NA
MODEL_2	2.50ns	NA	2.0ns	NA

results


Push-pull




|Model_name| Rise_on_dly | Rise_off_dly

MODEL_1	0.00ns	NA	0.00ns	NA	NA
MODEL_2	0.00ns	NA	2.50ns	2.00ns	NA


1

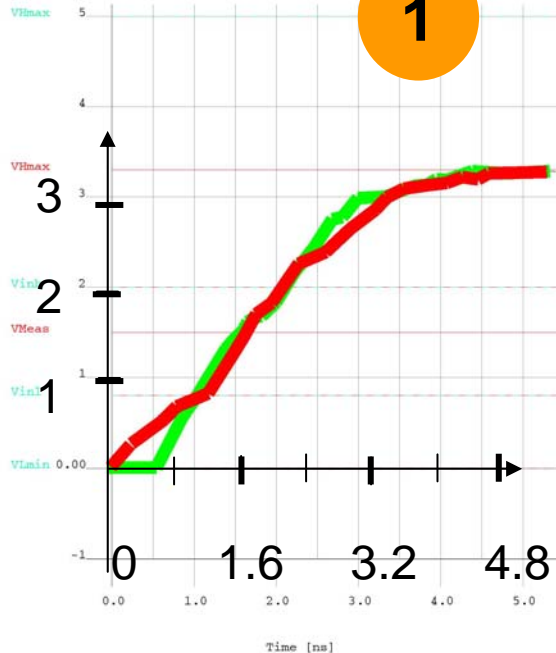

2

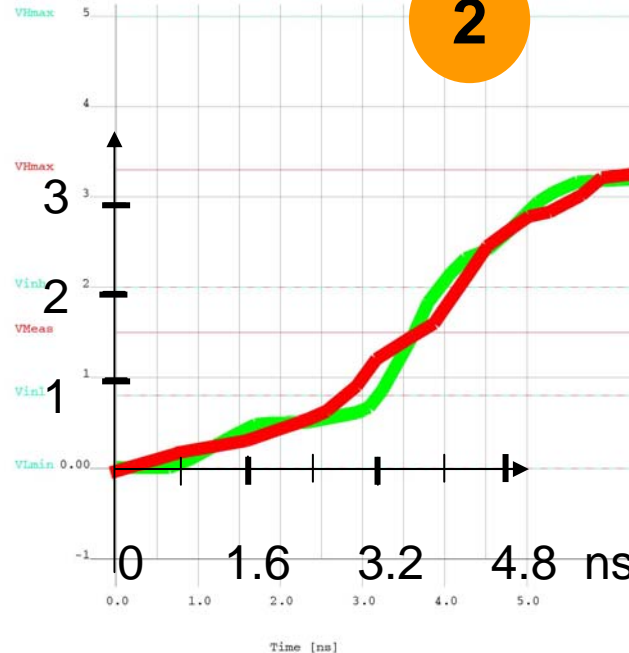

3

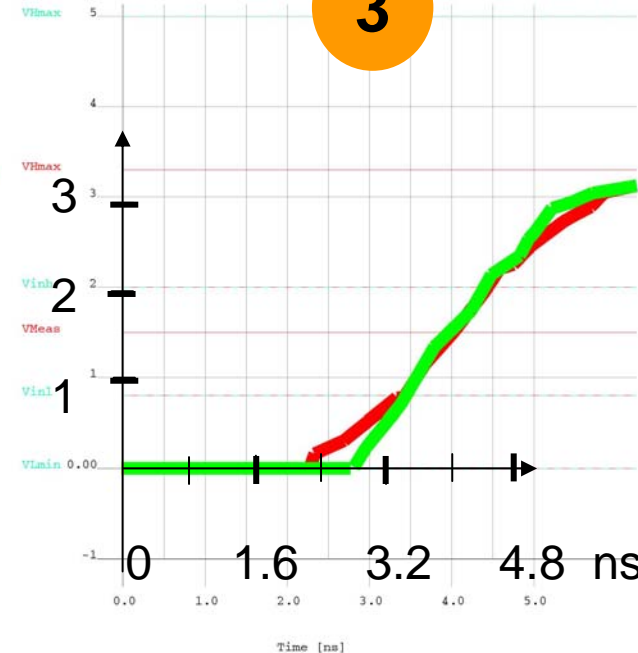

Testload was a 3 inch transmission line (open)

Driver



End of line




results with comments

Push-pull




Both drivers starting at time 0ns

1

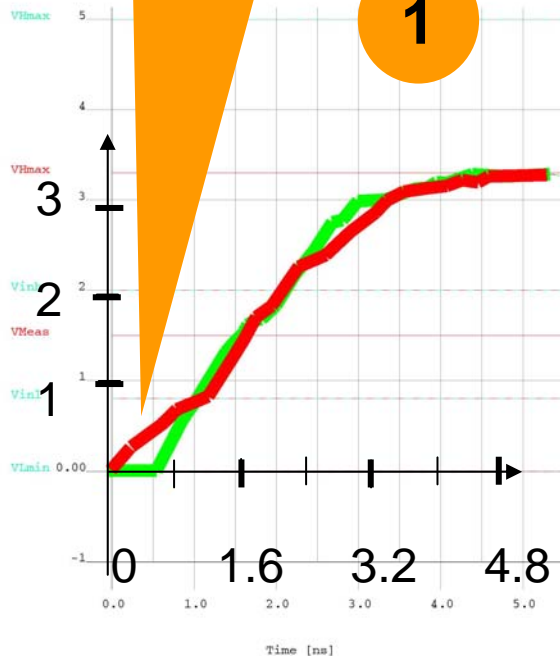


One driver starts at $t=0$ ns, the second driver starts at 2.5ns

2

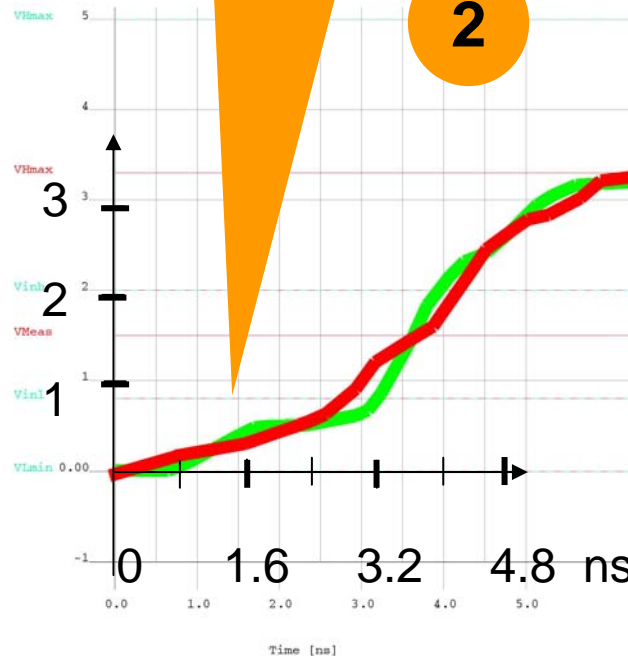

Both drivers starting with delaytime 2ns

3

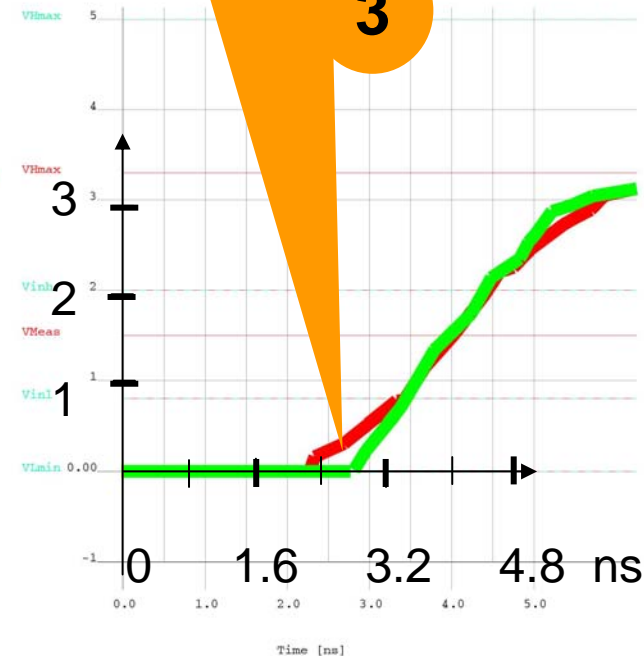

Testload was a 3 inch transmission line (open)

Driver



End of line



GTL-like driver schedules



IO models







GTL-like



Top level MODEL

MODEL_1

MODEL_2

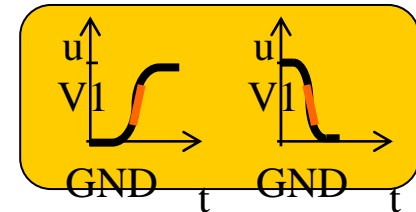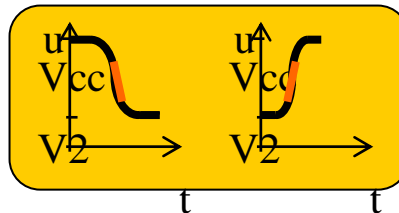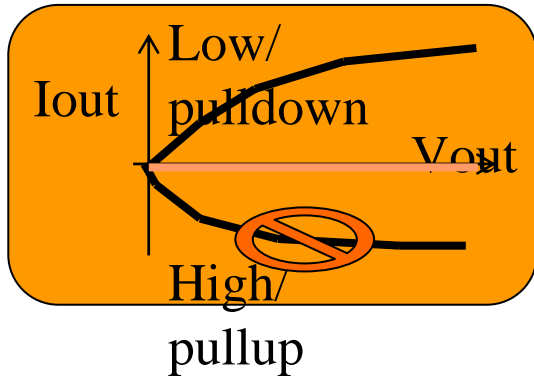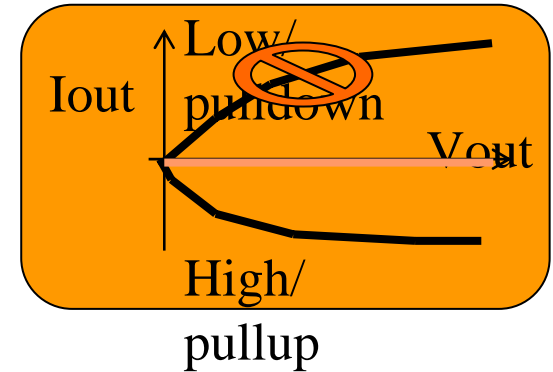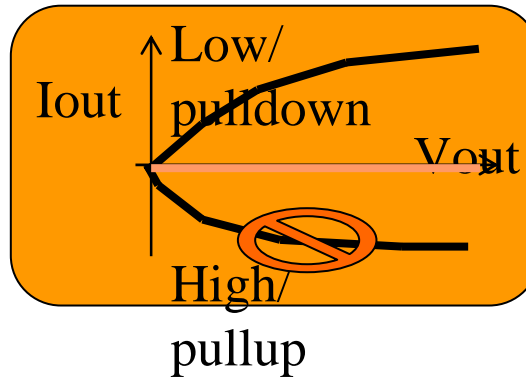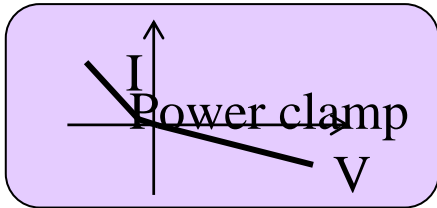

**Example with two IO-Models
and
with top level model information**

IBIS gtl driver schedule



[Driver schedule]

|Model_name Rise_on_dly Rise_off_dly Fall_on_dly Fall_off_dly

MODEL_OPSINK 0.00ns NA 2.0ns NA

MODEL_OPSOURCE 0.00ns 2.0ns NA NA

[pullup]

0.0V 0mA

[pulldown]

0.0V 0mA

2.0 35mA

[powerclamp]

0.0V 0mA

2.0V -10mA

[ramp] 0.5V/0.45ns

3 test cases



(here only rising edge shown)

Pulldown

1

Power clamp

Ramp

2

Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
MODEL_1	0.00ns	NA	2.0ns	NA
MODEL_2	0.00ns	2.0ns	2.0ns	NA





3

Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
MODEL_1	0.00ns	NA	2.0ns	NA
MODEL_2	0.00ns	2.0ns	2.0ns	NA

models overview for testcases

1

Case 1 top level

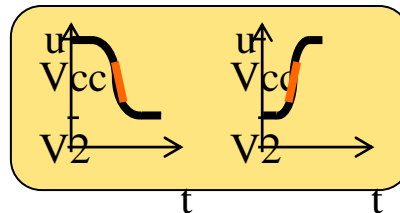
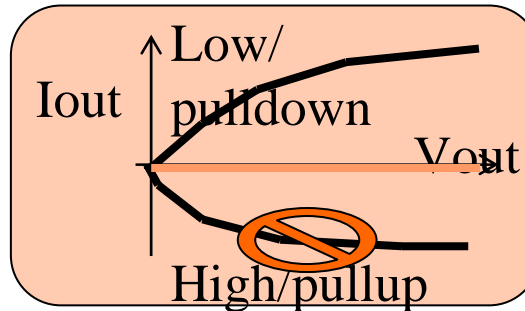
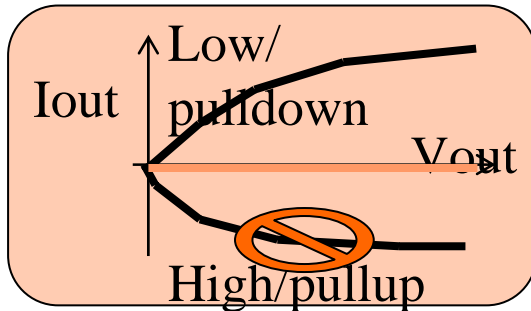
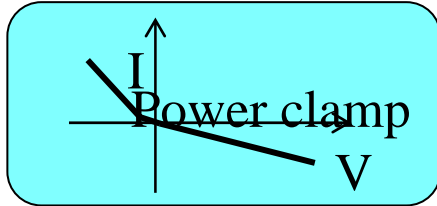


2

Case 2 Main only

3

Case 3 scheduled

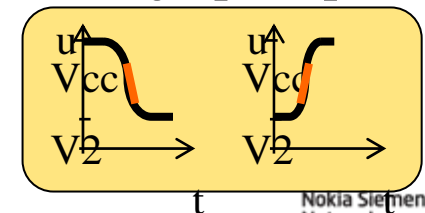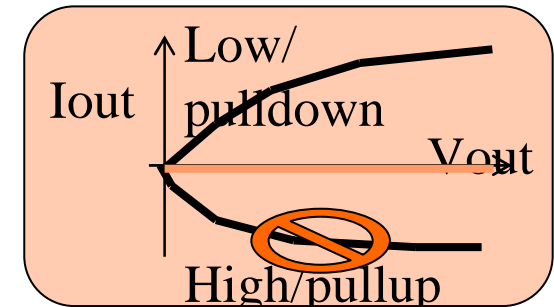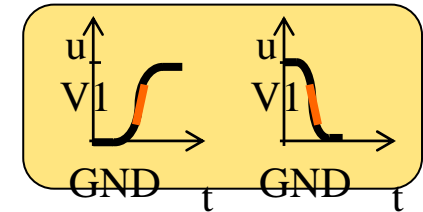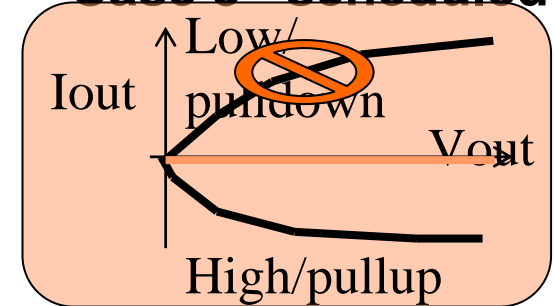

Nokia Siemens Networks

results

GT-like



Pulldown

Power clamp

|Model_name Rise_on_dly Rise_off_dly

MODEL_1 0.0ns NA

|Model_name Rise_on_dly Rise_off_dly




MODEL_1 0.0ns NA

MODEL_2 0.0ns 2.0ns

1

2

3

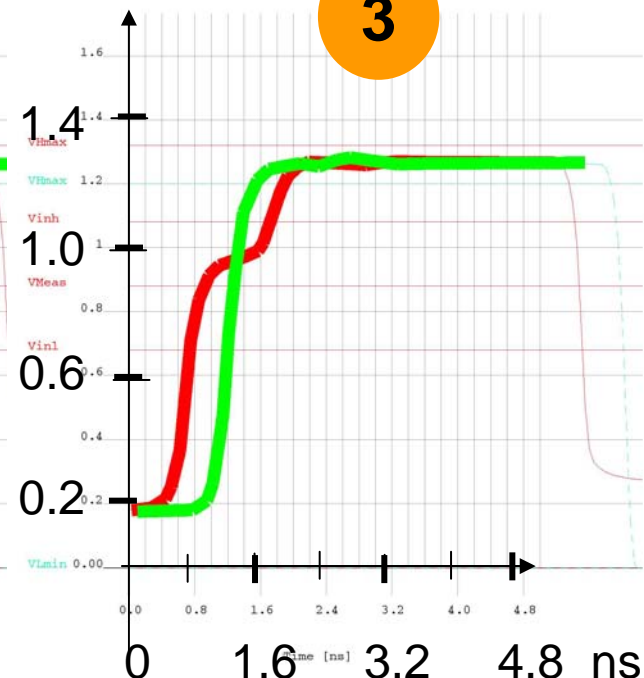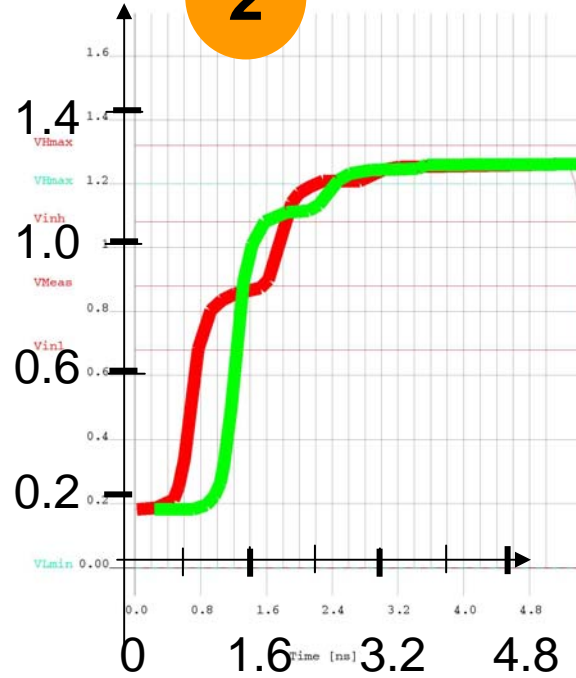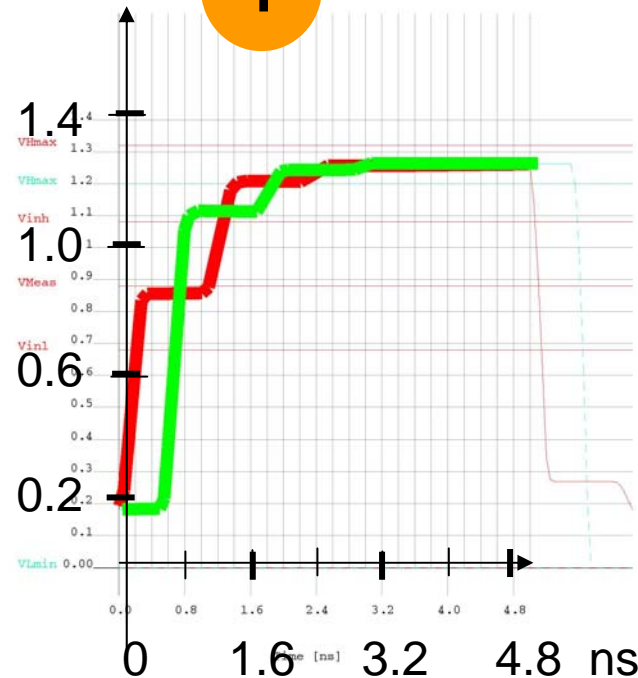

Testload was a 3 inch transmission line with Rload 50 to 1P2V

Driver



End of line




results with comments

GTL-like




Ramp only
no accurate rising

1

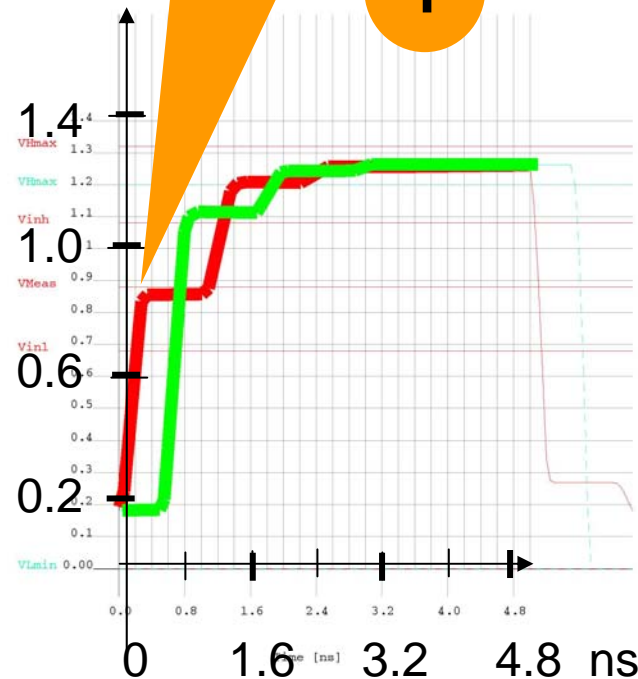


rising behavior from
external termination

2

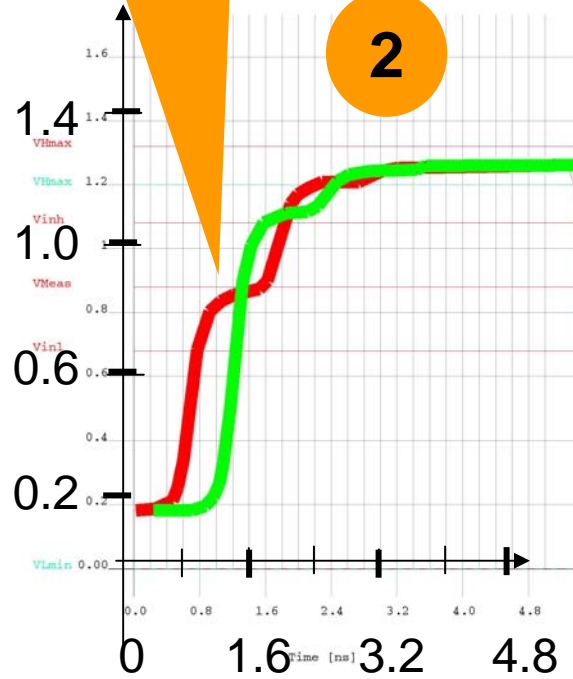

Additional swing by
open source driver

3

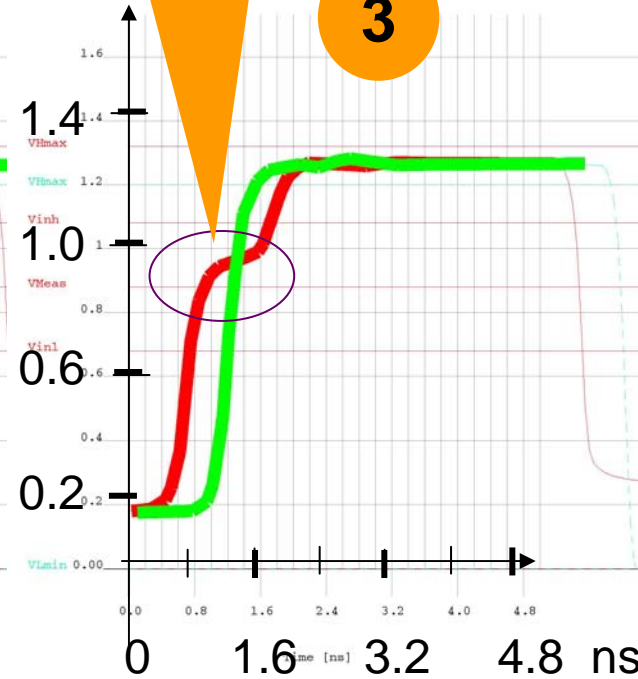


Testload was a 3 inch transmission line with Rload 50 to 1P2V

Driver — End of line



CML pre-emphasis

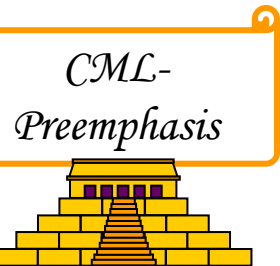









IO models



Top level MODEL

MODEL_1

MODEL_2

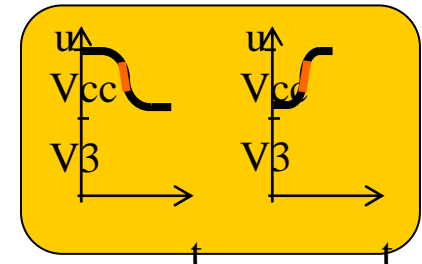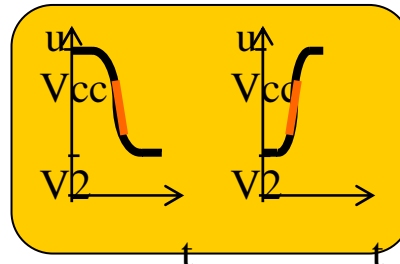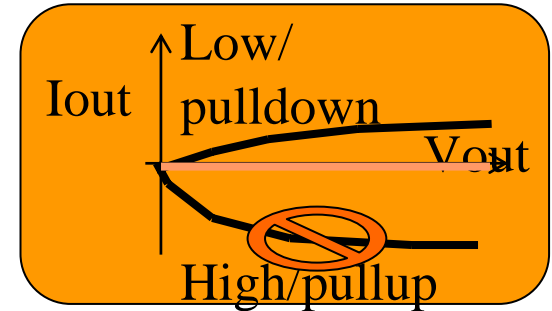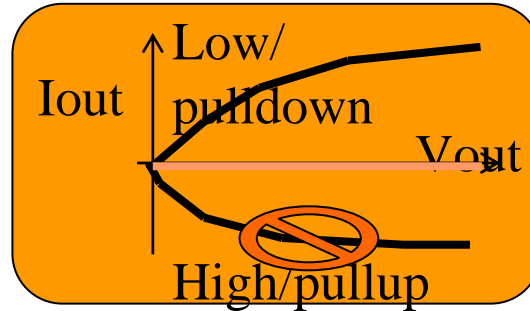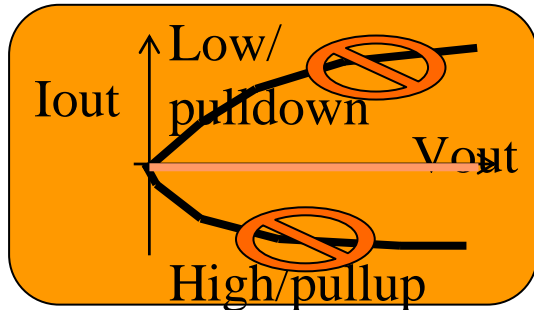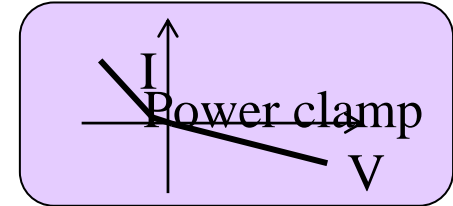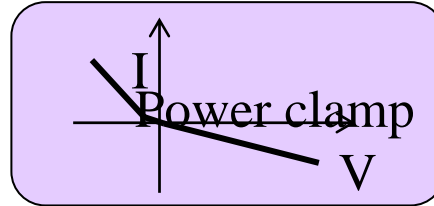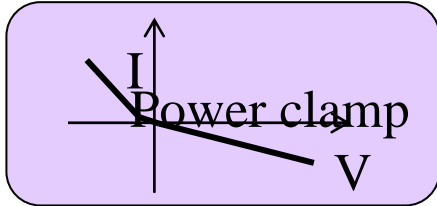

**Example with two IO-Models and
with wrong top level model information**

IBIS cml driver schedule



[Driver schedule]

[Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
MODEL_OPSINKMAIN		0.00ns	NA	2.0ns
MODEL_OPSINKBOOST		0.00ns	0.8ns	NA

[pullup]

0.0V 0mA

[pulldown]

0.0V 0mA

2.0V 0mA

[powerclamp]

0.0V 0mA

2.0V -10mA

[ramp] 0.4V/37ps

3 test cases



(here only rising edge shown)

Pulldown

1

Power clamp

Ramp

2

Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
MODEL_MAIN	0.00ns	NA	2.0ns	NA
MODEL_BOOST	0.00ns	0.8ns	2.0ns	NA

3

Model_name	Rise_on_dly	Rise_off_dly	Fall_on_dly	Fall_off_dly
MODEL_MAIN	0.00ns	NA	2.0ns	NA
MODEL_BOOST	0.00ns	0.8ns	2.0ns	NA

models for test cases

1












2

3

Case 1 top level

Case 2 Main only

Case 3 scheduled

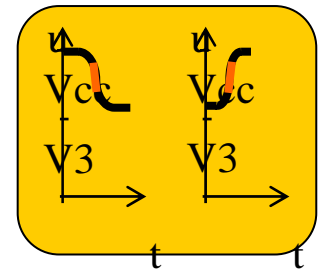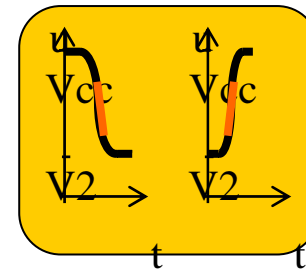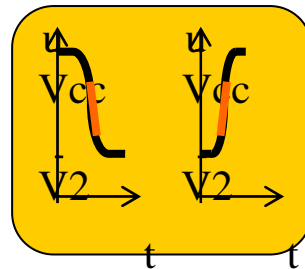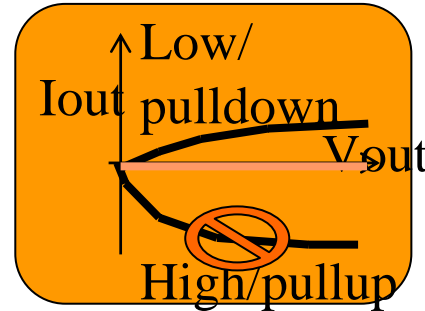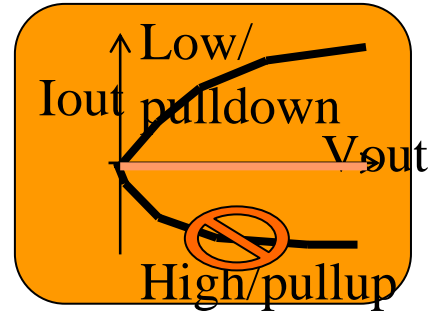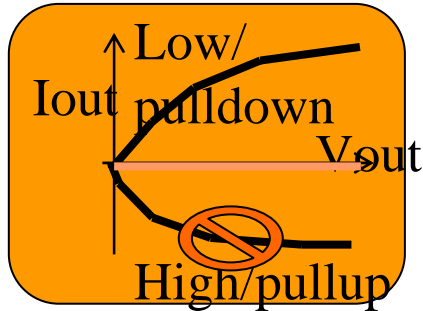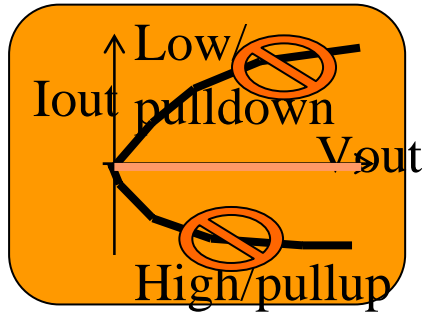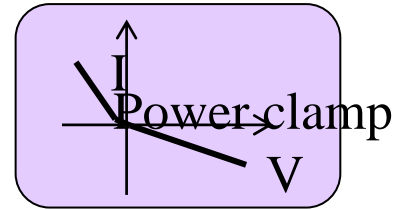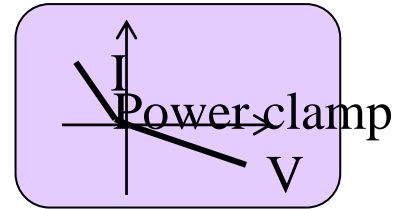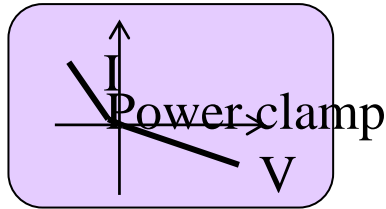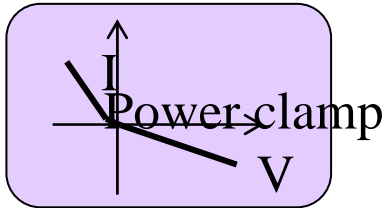

results

CML-
Preemphasis






2

3

1

Model_name	Rise_on_dly	Rise_off_dly
MODEL_1	0.0ns	NA

Model_name	Rise_on_dly	Rise_off_dly
MODEL_1	0.0ns	NA
MODEL_2	0.0ns	0.8ns

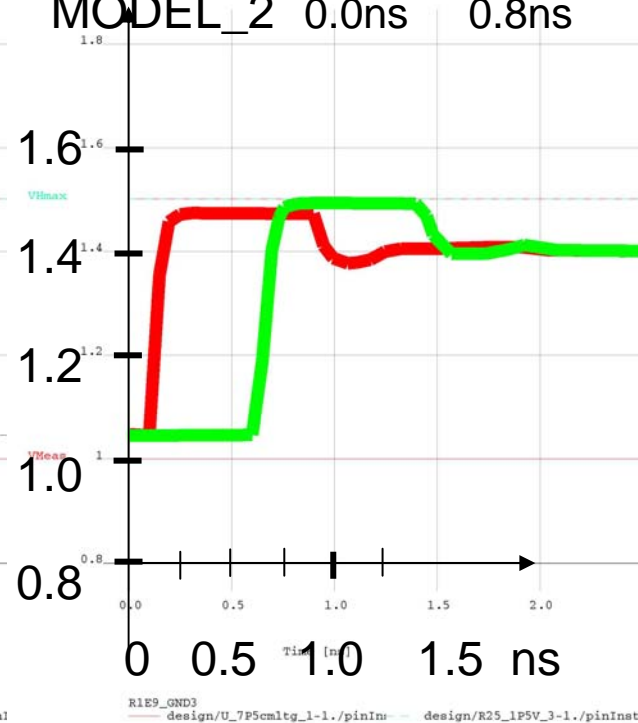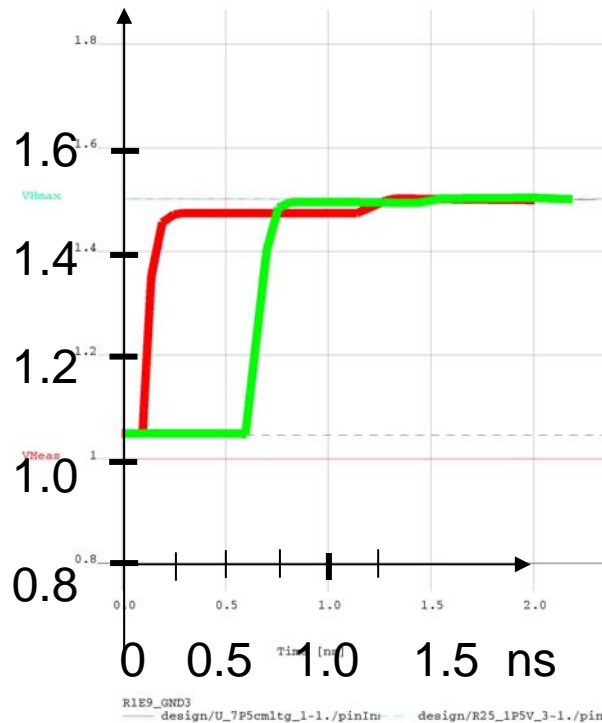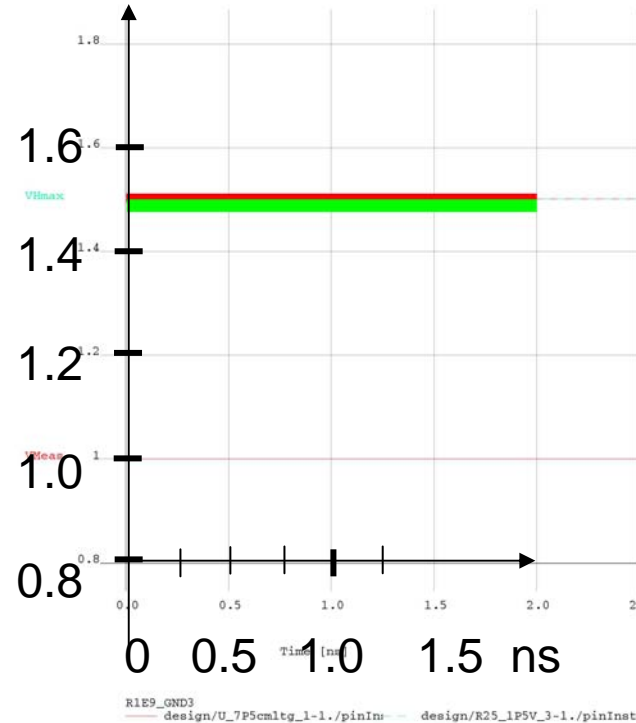

Testload was a 3 inch transmission line with Rload 50 to 1P5V


Driver — End of line —



results with comments


No switching at all

1

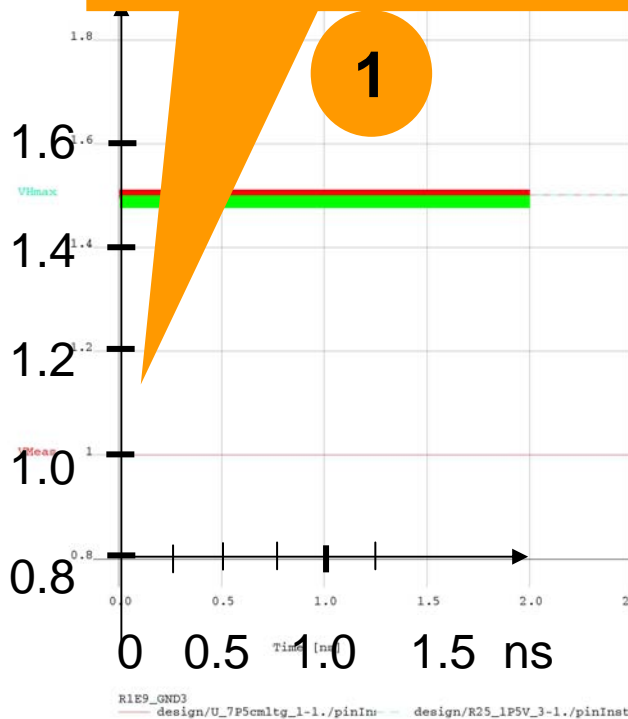


Switches up to 1.5V
Correct level, but no
pre-emphasis ?

2

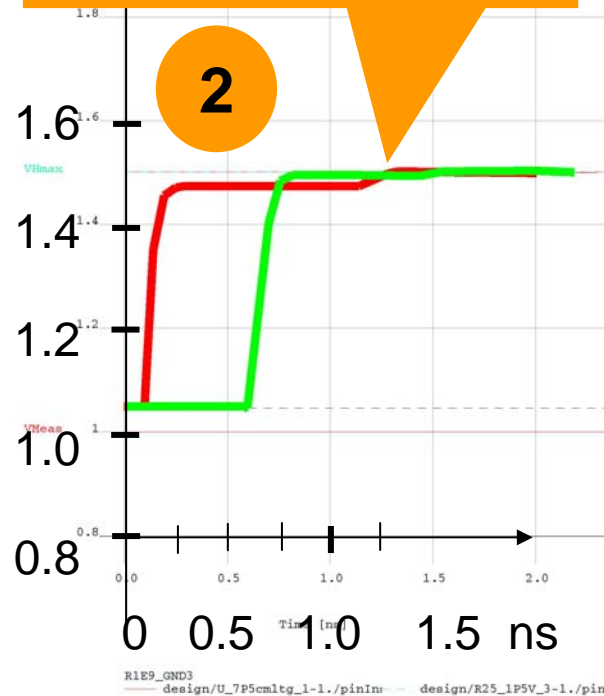

Shows Pre-emphasis
behavior, but then goes
back to 1.4V ??

3

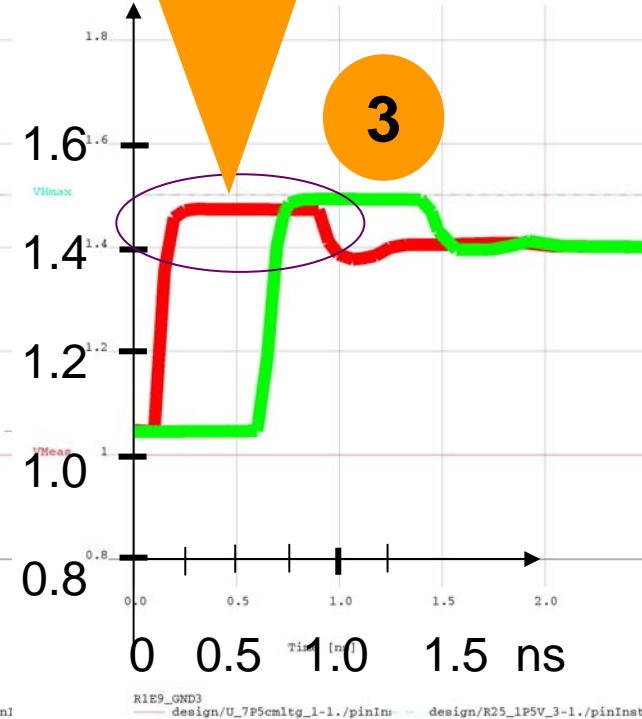

Testload was a 3 inch transmission line with Rload 50 to 1P5V

Driver — End of line —

Summary

- Timing dependant drivers works fine
- Voltage dependant drivers should be possible with [submodel] and ,fall-back‘
- Pre-emphasis modeling is possible, but only with fixed ,Pre-emphasis‘
- Pattern dependant ,Pre-emphasis‘ with VHDL-AMS
- Check of combined static and dynamic waveforms necessary
- Driver schedule models have to be carefully checked



Thank You

• **Questions ?**