



Driver Schedule Modeling

Christopher E. Reid and Bob Ross

**IBIS Summit Meeting
Las Vegas, Nevada**

June 21, 2001

Contents


- **Driver Schedule Enhancement and Reduction Setups**
- **Possible Improvement for Over-clocked mode where start of next transition is before the finish of previous transition**
- **Application for SCSI**
- **Illustration of Driver Schedule for Discrete Waveform Shaping**

Driver Schedule Examples

(D6 is not legal - ambiguous)

Name	Rise-on	Rise-off	Fall-on	Fall-off
D1	0	na	0	na
D2	na	0	na	0
D3	0	5ns	na	na
D4	5ns	0	na	na
D5	na	na	3ns	5ns
D6	0	5ns	0	5ns

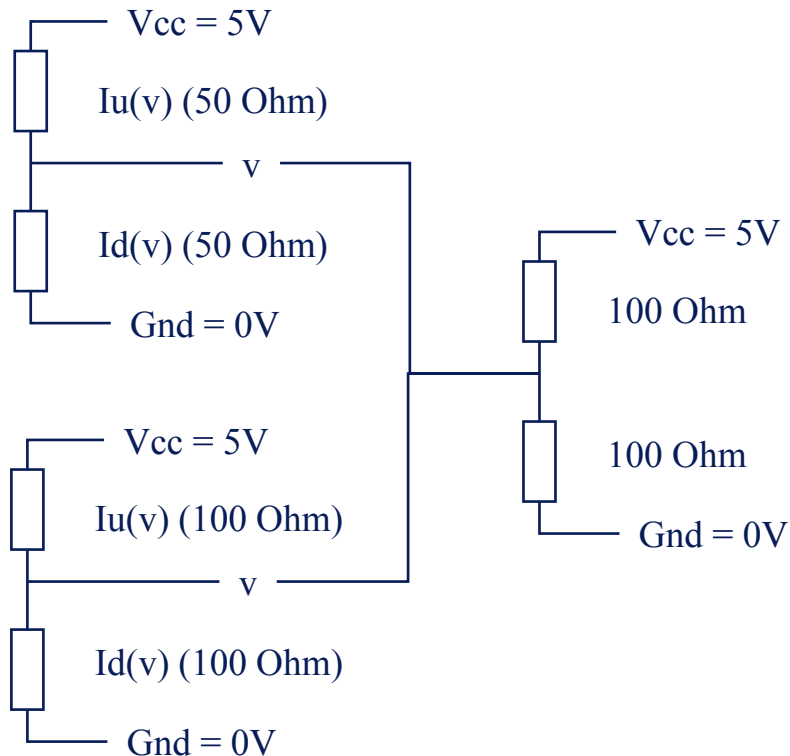Driver Schedule Test Circuit (Produces 1, 2, 3, 4 V outputs)



<i>Name</i>	<i>50-Ohm</i>	<i>100-Ohm</i>	<i>V</i>
Ls	Low	Low	1
Lw	Low	High	2
Hw	High	Low	3
Hs	High	High	4

Valid Setup Examples for Enhancement and Reduction

<i>Driver</i>	<i>Rise-on</i>	<i>Rise-off</i>	<i>Fall-on</i>	<i>Fall-off</i>
D_50	0ns	na	0ns	na
D_100	1ns	na	1ns	na

<i>Driver</i>	<i>Rise-on</i>	<i>Rise-off</i>	<i>Fall-on</i>	<i>Fall-off</i>
D_50	0ns	na	0ns	na
D_100	na	1ns	na	1ns

<i>Driver</i>	<i>Rise-on</i>	<i>Rise-off</i>	<i>Fall-on</i>	<i>Fall-off</i>
D_50	0ns	na	0ns	na
D_100	1ns	4ns	na	na

<i>Driver</i>	<i>Rise-on</i>	<i>Rise-off</i>	<i>Fall-on</i>	<i>Fall-off</i>
D_50	0ns	na	0ns	na
D_100	4ns	1ns	na	na

SCSI Driver Example Using Reduced Strength Driver


<i>Driver</i>	<i>Rise-on</i>	<i>Rise-off</i>	<i>Fall-on</i>	<i>Fall-off</i>
D_50	0ns	na	0ns	na
D_100	na	5ns	na	5ns

<i>Driver</i>	<i>Rise-on</i>	<i>Rise-off</i>	<i>Fall-on</i>	<i>Fall-off</i>
D_50	0	na	0ns	na
D_100	0	5ns	0	5ns


■ Two versions of the SCSI Driver

- Version 1 is legal IBIS - next page
- Version 2 is not legal, but responds more cleanly to over-clocking. However the pulse widths are not made narrower and are wrong - page after next.

Valid Second Bit Reduction

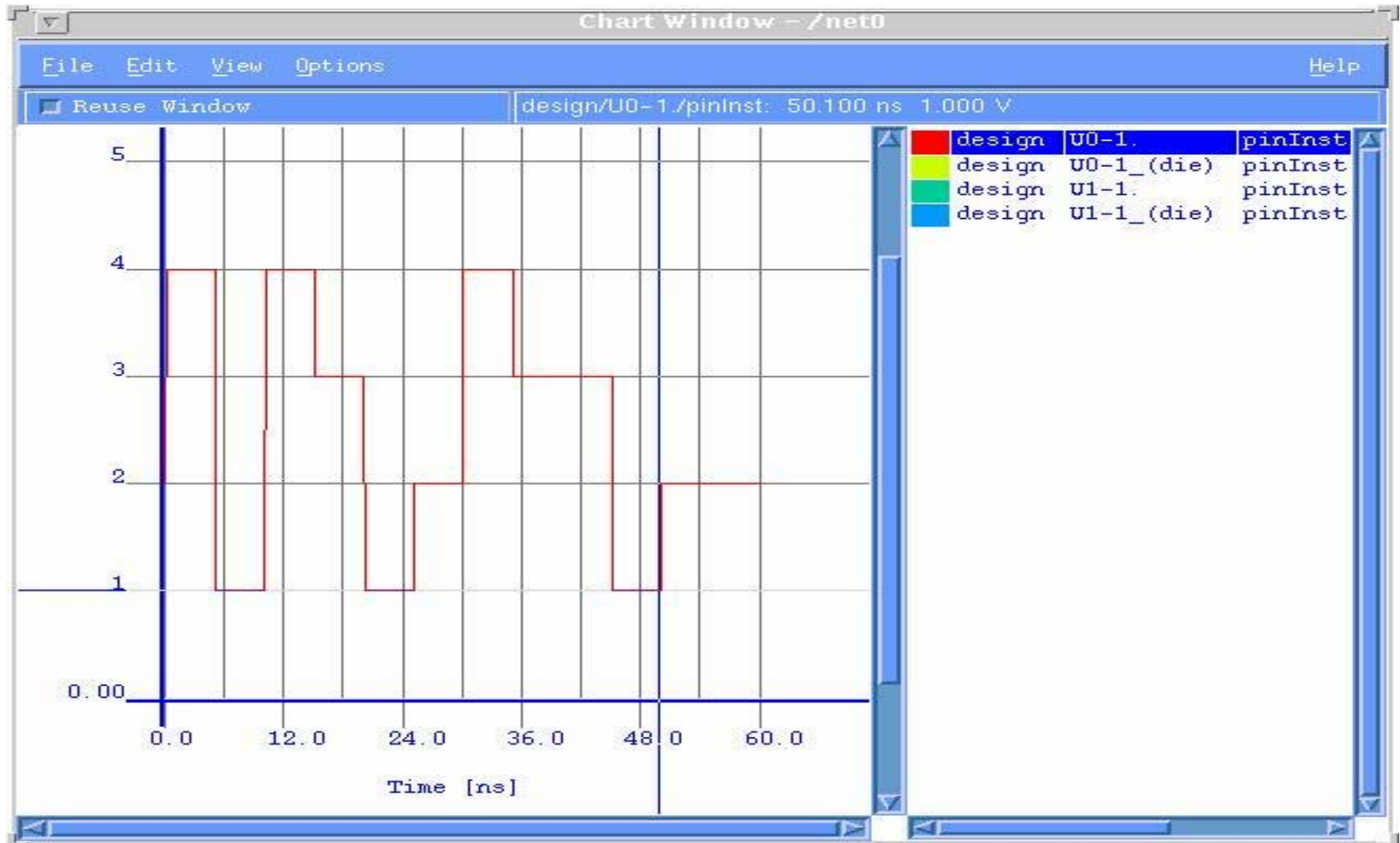

2-bits = 8 nS (but 5 nS pulse width)

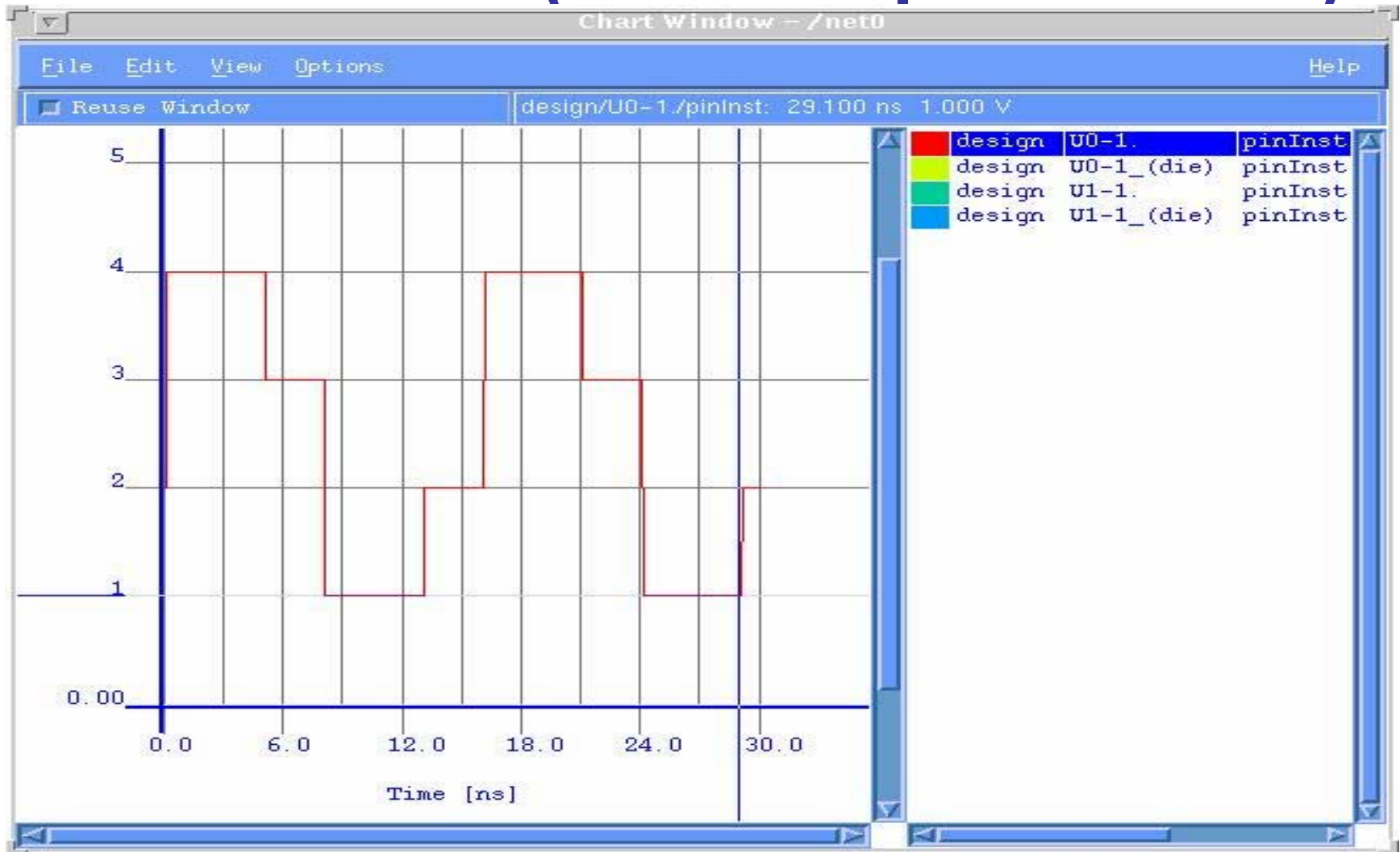

Stair Step Waveform Showing Enhancement and Reduction

- Drivers (9 V)
 - U0 - 25 Ohm - Output
 - U1 - 50 Ohm - Open_drain and Open_source
 - U2 - 100 Ohm - Open_drain and Open_source
 - Open_* used because of several transitions in “Rise_*” and “Fall_*” pulse
- Terminator - 100 Ohm 9V, 100 Ohm Gnd
- 1 V to 8 V in 1 V Steps

```

| *****
|
|          typ          min          max
[Voltage range]      9V          NA          NA
|
| *****
|
[Driver Schedule]
|  Model          Rise_on  Rise_off  Fall_on  Fall_off
U0                      0        7n        NA        NA

U1_UP                  2n        5n        NA        NA
U1_DOWN                2n        0n        NA        NA
U1_DOWN                7n        5n        NA        NA


U1_UP                  NA        NA        2n        0n
U1_UP                  NA        NA        7n        5n
U1_DOWN                NA        NA        2n        5n

U2_UP                  1n        2n        NA        NA
U2_UP                  3n        4n        NA        NA
U2_UP                  5n        6n        NA        NA
U2_DOWN                1n        0n        NA        NA
U2_DOWN                3n        2n        NA        NA
U2_DOWN                5n        4n        NA        NA
U2_DOWN                7n        6n        NA        NA

U2_UP                  NA        NA        1n        0n
U2_UP                  NA        NA        3n        2n
U2_UP                  NA        NA        5n        4n
U2_UP                  NA        NA        7n        6n
U2_DOWN                NA        NA        1n        2n
U2_DOWN                NA        NA        3n        4n
U2_DOWN                NA        NA        5n        6n

```

Pulse Width 7 nS, Period 14 nS

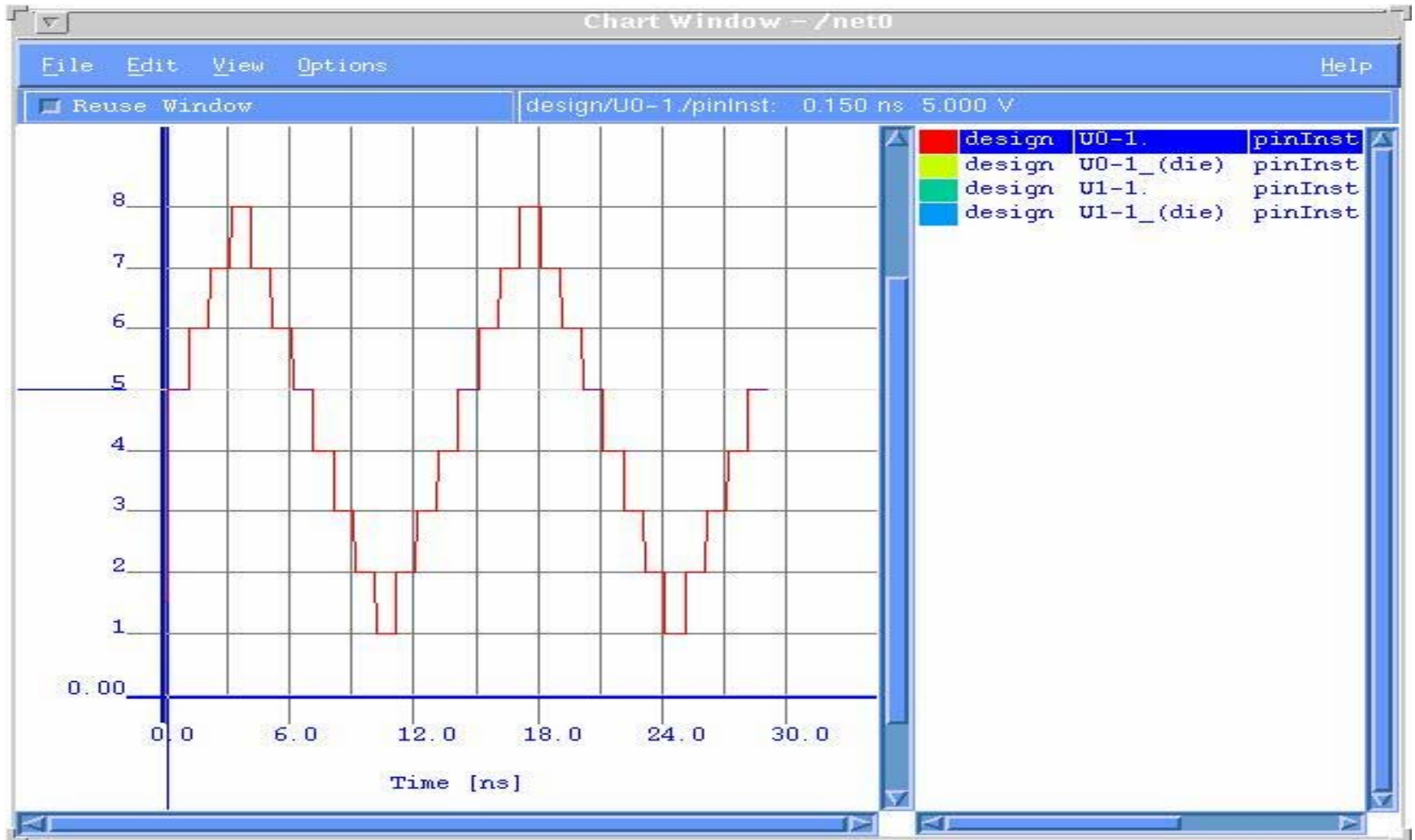

Driver Schedule Observations

- Existing Driver Schedule can be used for second bit reduction for SCSI applications for a given clock rate.
- Allowing another Driver Schedule mode produces some improvement, but produces other distortions. This improvement is not recommended.
- Driver Schedules with Open_* modes can be used for discrete pulse shaping.