

Characterizing and Modeling of a Linear CTE

Skipper Liang


Asian IBIS Summit

Shanghai, PRC

November 13, 2017

To Divide a RX Circuit:

 For modeling a RX circuit, we usually need to separate the whole design into buffer part and algorithm part:



1. Question 1: What's the value of **Z1** and **Z2**?
2. Question 2: What if the whole design is described in **an encrypted netlist**?

IBIS model

- generated from AMI generation tools

Name ^	Date modified	Type	Size
SRC	8/11/2017 4:23 PM	File folder	
build_ami.log	8/11/2017 4:24 PM	LOG File	5 KB
cdns_tx_rx.ibs	8/11/2017 4:24 PM	IBS File	3 KB
Rx1.ami	8/11/2017 4:23 PM	AMI File	3 KB
Rx1.dll	8/11/2017 4:24 PM	Application extension	3,321 KB
Rx1.module	8/11/2017 4:23 PM	MODULE File	1 KB
Rx1.module.wiz	8/11/2017 4:23 PM	Microsoft Word Wiz...	1 KB

Many AMI generation tools will generate an IBIS model along with the AMI models generation:

1. Question 1: Can we use this IBIS model? **YES**
2. Question 2: If yes, is there any requirement of the circuit while modeling this circuit in this way?

The circuit should be a RX one composed of linear components.

3. Question 3: If my circuit could meet the requirement list above, how to do the modeling?

Detailed in the following pages

Thevenin's Theorem

Thévenin's theorem


From Wikipedia, the free encyclopedia

As originally stated in terms of DC [resistive](#) circuits only, **Thévenin's theorem** holds that:

- Any [linear electrical network](#) with [voltage](#) and [current sources](#) and only [resistances](#) can be replaced at terminals A-B by an equivalent voltage source V_{th} in [series](#) connection with an equivalent resistance R_{th} .
- The equivalent voltage V_{th} is the voltage obtained at terminals A-B of the network with terminals A-B [open circuited](#).
- The equivalent resistance R_{th} is the resistance that the circuit between terminals A and B would have if all ideal voltage sources in the circuit were replaced by a short circuit and all ideal current sources were replaced by an open circuit.
- If terminals A and B are connected to one another, the current flowing from A to B will be V_{th}/R_{th} . This means that R_{th} could alternatively be calculated as V_{th} divided by the short-circuit current between A and B when they are connected together.

In [circuit theory](#) terms, the theorem allows any [one-port](#) network to be reduced to a single [voltage source](#) and a single impedance.

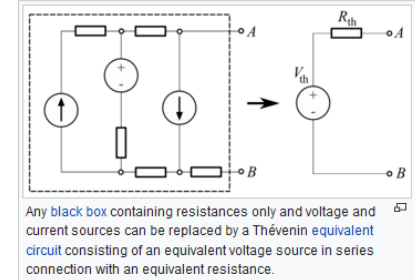The theorem also applies to frequency domain AC circuits consisting of [reactive](#) and [resistive impedances](#). It means the theorem applies for AC in an exactly same way to DC except that resistances are generalized to impedances.



In short:


V_{TH} = The voltage across the Port – “node A and B” while treating the Port – “node A and B” as **OPEN**

I_{SC} = The current goes into node A and leaves node B while treating the Port – “node A and B” as **SHORT**

$$R_{TH} = V_{TH}/I_{SC}$$


Thevenin Equivalence

Typically, an RX test topology

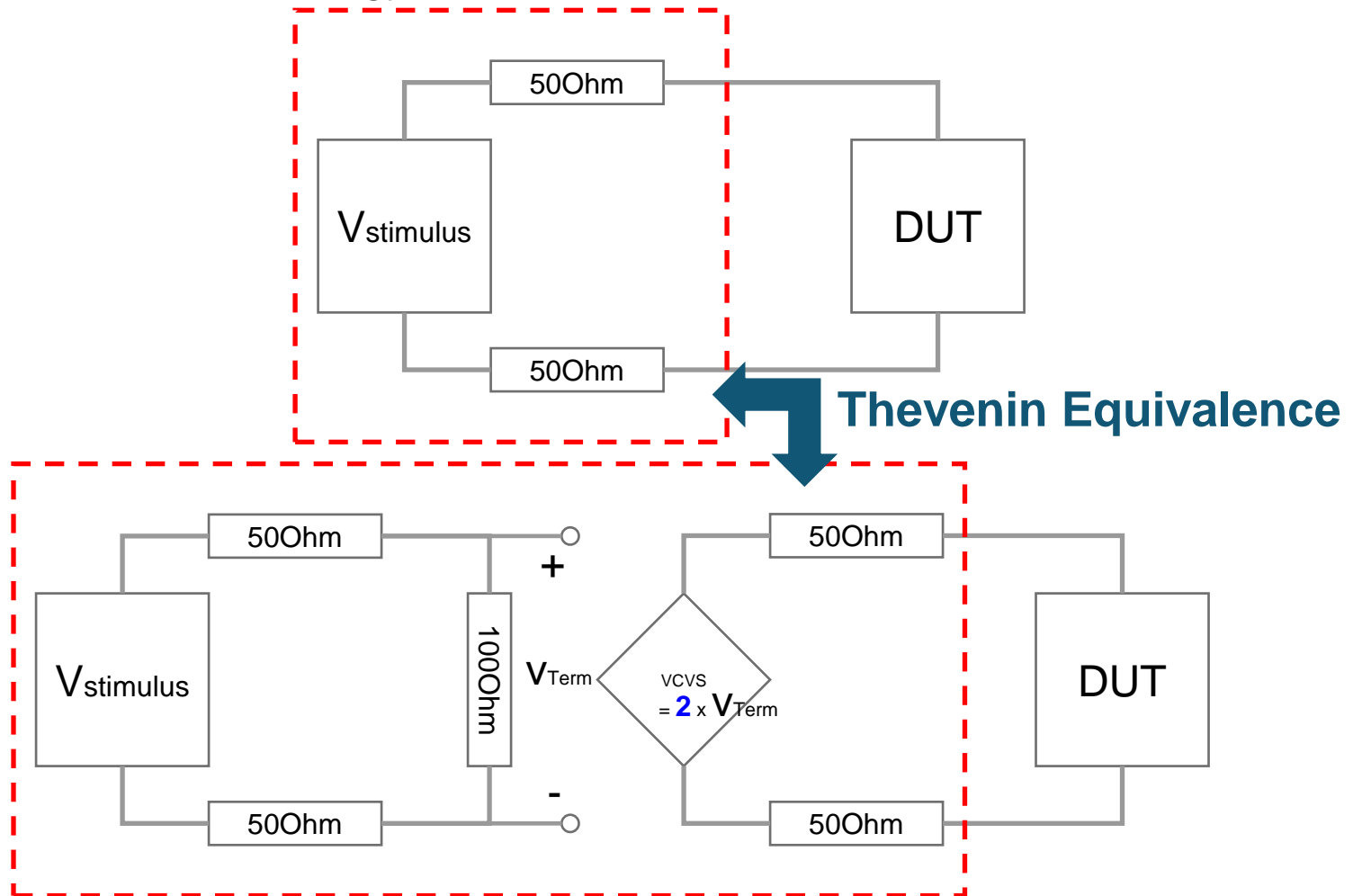





Thevenin Equivalence(Cont'd)

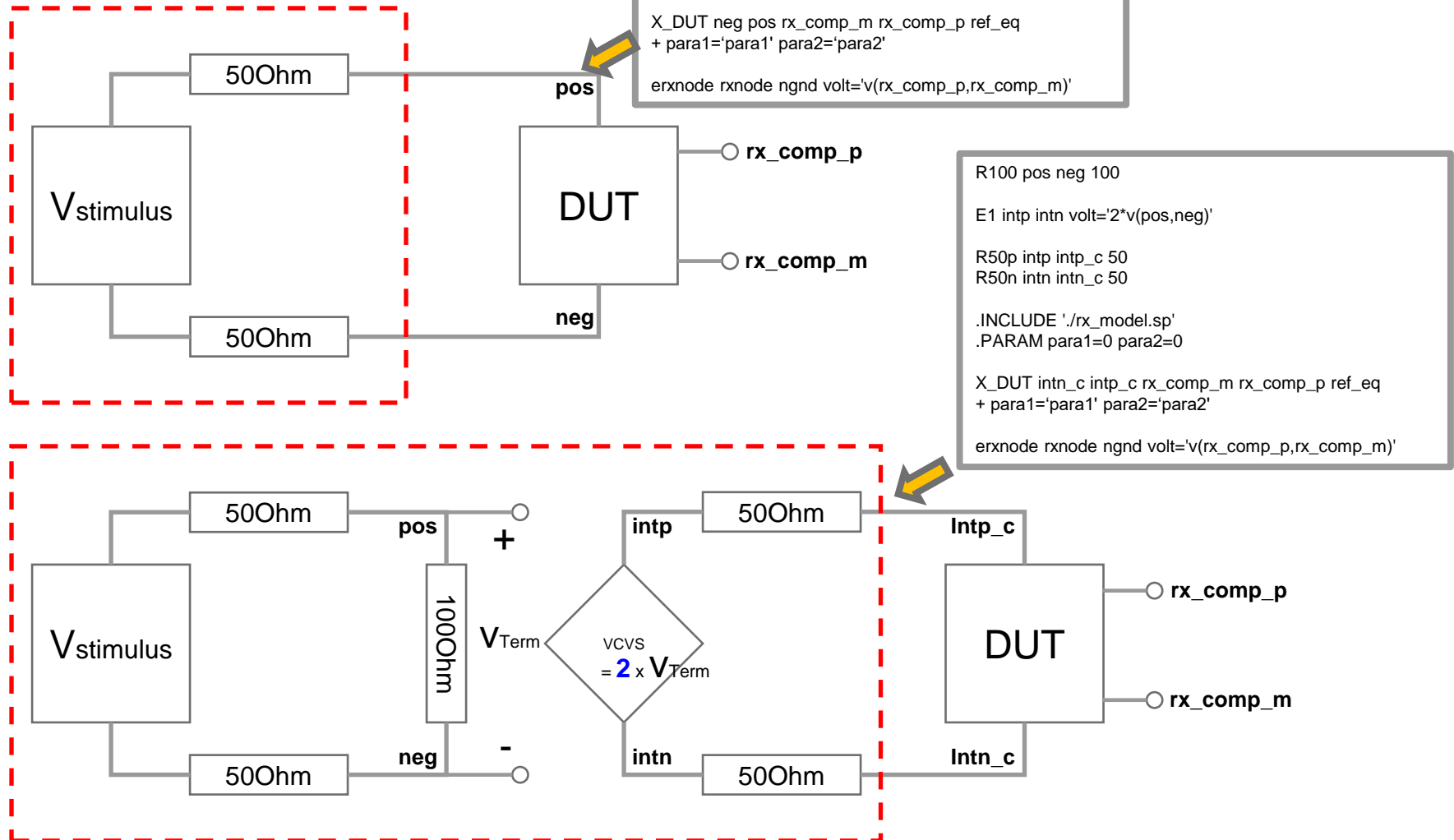You can do a small experiment – the following 2 netlist will give the same waveform result at the EQ's output




Thevenin Equivalence(Cont'd)

Hard to tell the difference

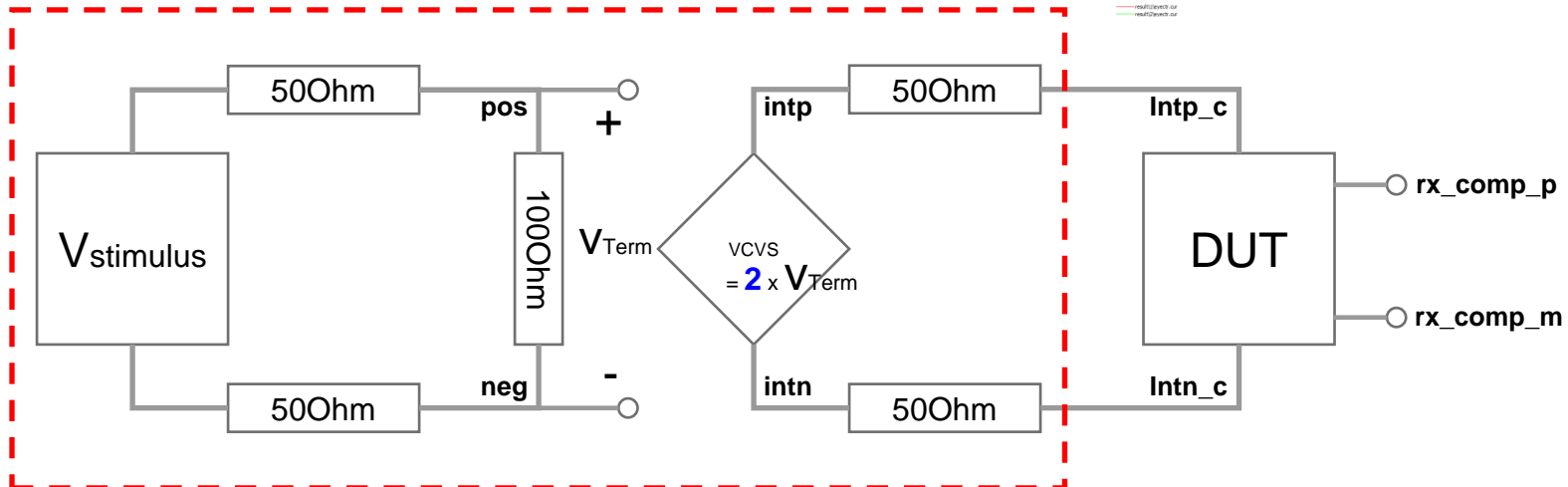  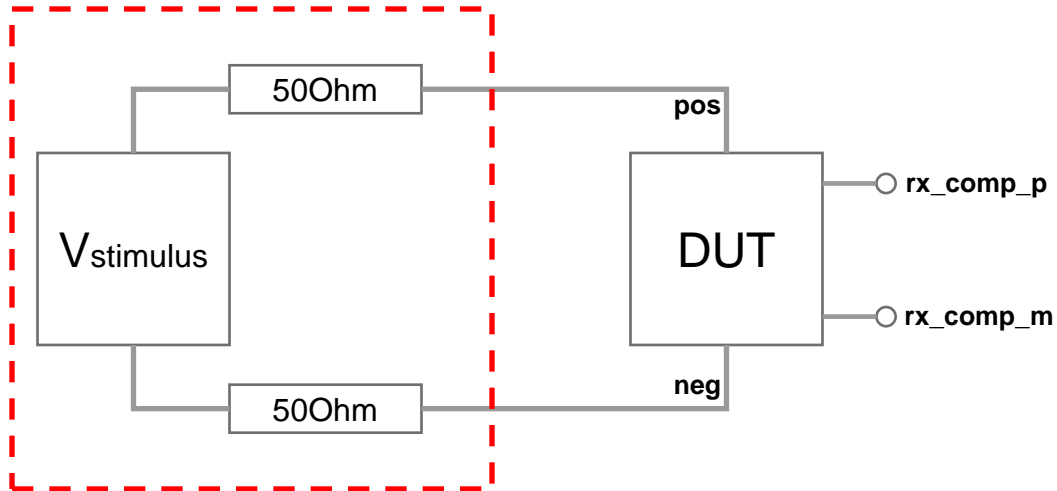

Alternative RX

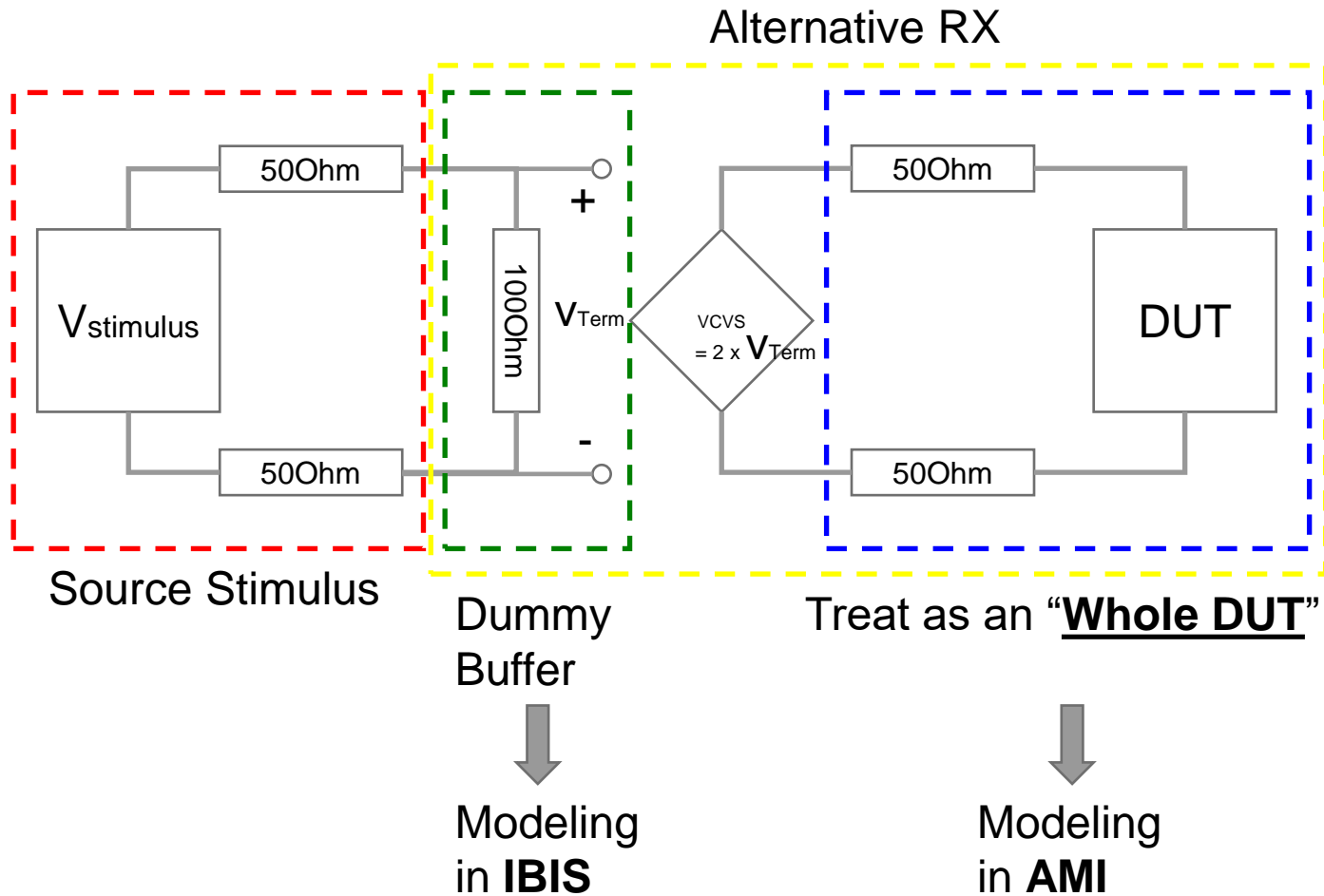


IBIS of the Dummy Buffer

Check the RX IBIS model, which is generated along with the AMI model, to see if it's a 100Ohm terminator between positive node and negative node:


Name ^	Date modified	Type	Size
 SRC	3/17/2017 3:30 PM	File folder	
 build_ami	3/17/2017 3:30 PM	LOG File	5 KB
 cdns_tx_rx	3/17/2017 3:30 PM	IBS File	3 KB

 For example, some AMI generation tools generate RX IBIS model with 90Ohm terminator between positive node and negative node – tell from the [Power Clamp] and [Ground Clamp]:



Alternative RX for a 90Ohm terminator


Alternative RX

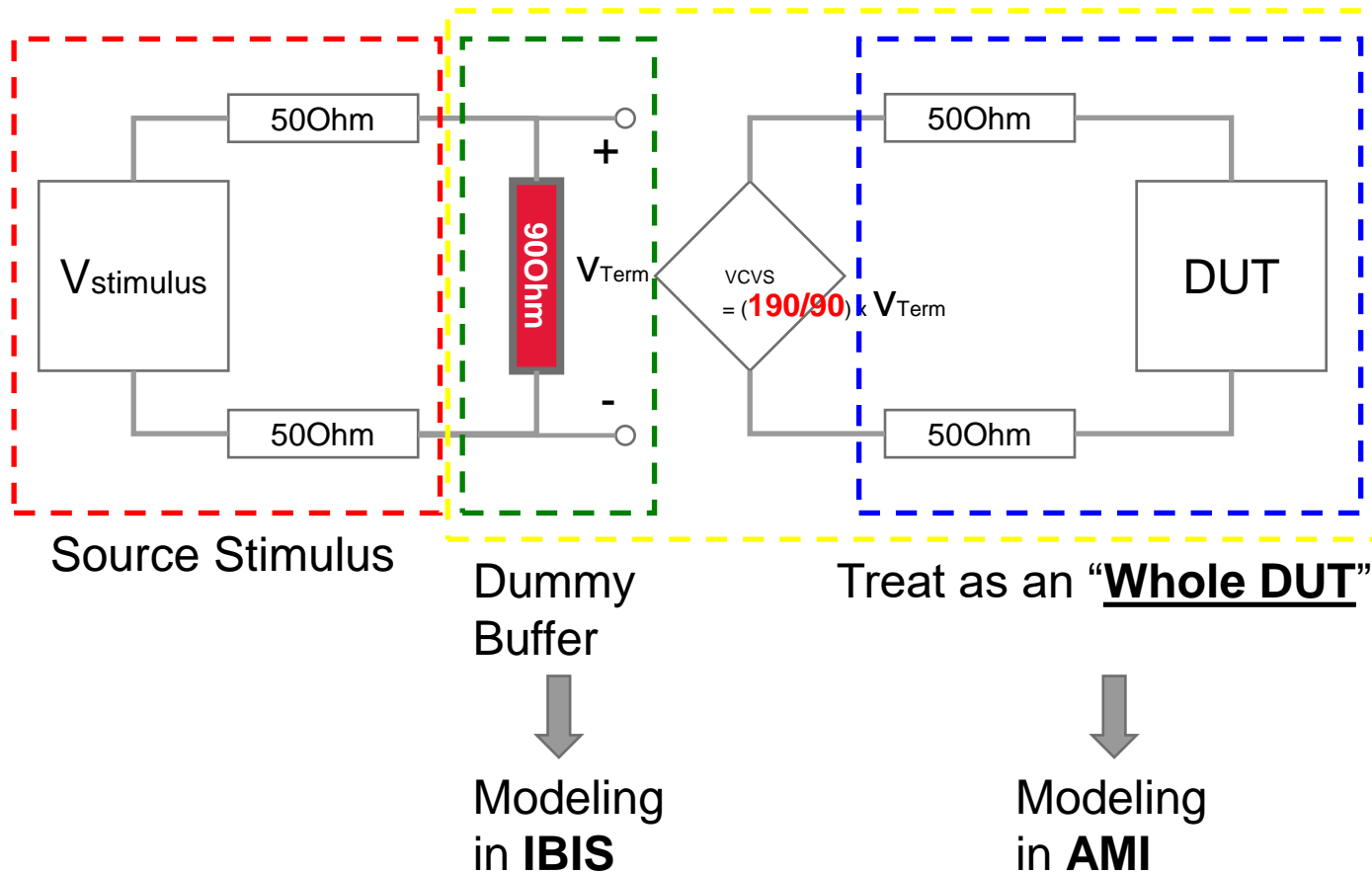

Or.....

IBIS model of 100Ohm terminator

Alternative RX

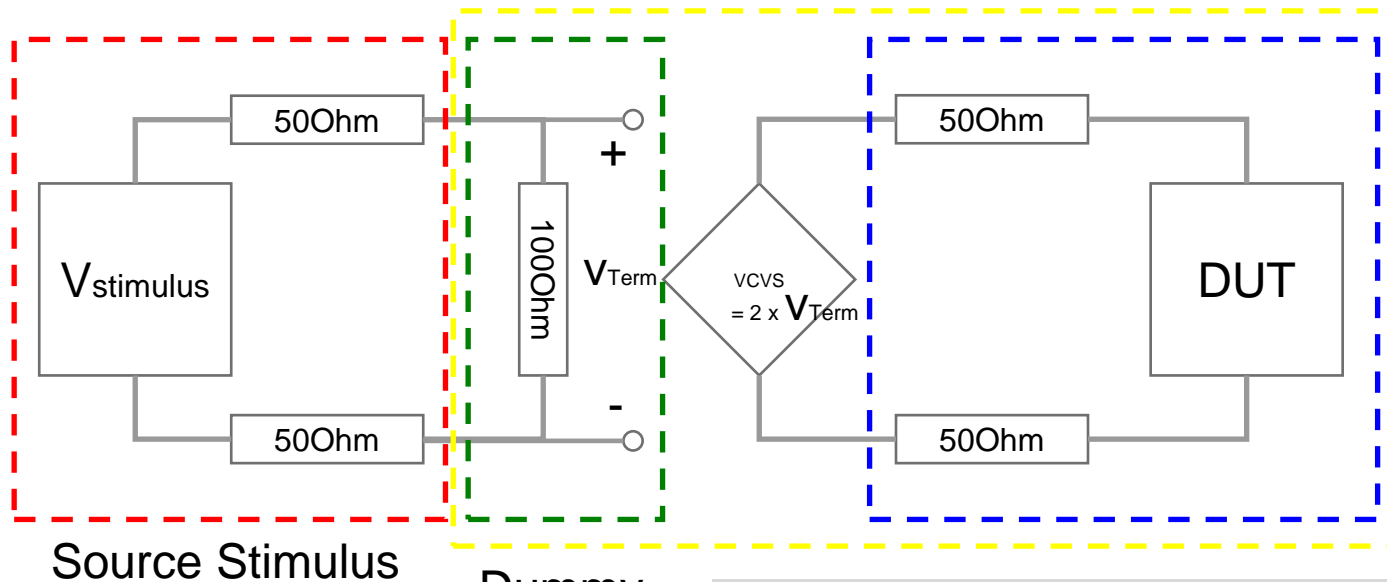

Source Stimulus

Dummy
Buffer

Modeling
in **IBIS**

And now, you don't need to model the IBIS part or use the non-100Ohm terminator IBIS model. You just use the files here attached:



rx100term.ibs



R_100.ckt

IBIS model of 100Ohm terminator (Cont'd)

The content of these files:



rx100term.ibs

```
[Model] RX
Model_type Input_diff
[Voltage Range] 1.000V 1.0V 1.0V
[Ramp]
| variable typ min max
dV/dt_r 0.120/0.001n 0.120/0.001n 0.120/0.001n
dV/dt_f 0.120/0.001n 0.120/0.001n 0.120/0.001n
R_load = 50.000
|
[External Model]
Language SPICE
|
| Corner corner_name file_name circuit_name (.subckt name)
Corner Typ R_100.ckt R_100
Corner Min R_100.ckt R_100
Corner Max R_100.ckt R_100
|
| Ports List of port names (in same order as in SPICE)
Ports A_puref A_pdref A_signal_pos A_signal_neg
|
| A_to_D d_port port1 port2 vlow vhigh corner_name
A_to_D D_receive A_signal_pos A_signal_neg -0.0 0.1 Typ
A_to_D D_receive A_signal_pos A_signal_neg -0.0 0.1 Min
A_to_D D_receive A_signal_pos A_signal_neg -0.0 0.1 Max
|
[End External Model]
[Algorithmic Model]
Executable Windows_VisualStudio_64 RX_HyperCore.dll RX_HyperCore.ami
[End Algorithmic Model]
|
[End]
```




R_100.ckt

```
1 .subckt R_100 DVDD DVSS pos neg
2
3 Rp pos gnd 1e+15
4 Rn neg gnd 1e+15
5 Rdiff pos neg 100
6
7 .ends
```

Characterizing:

Alternative RX

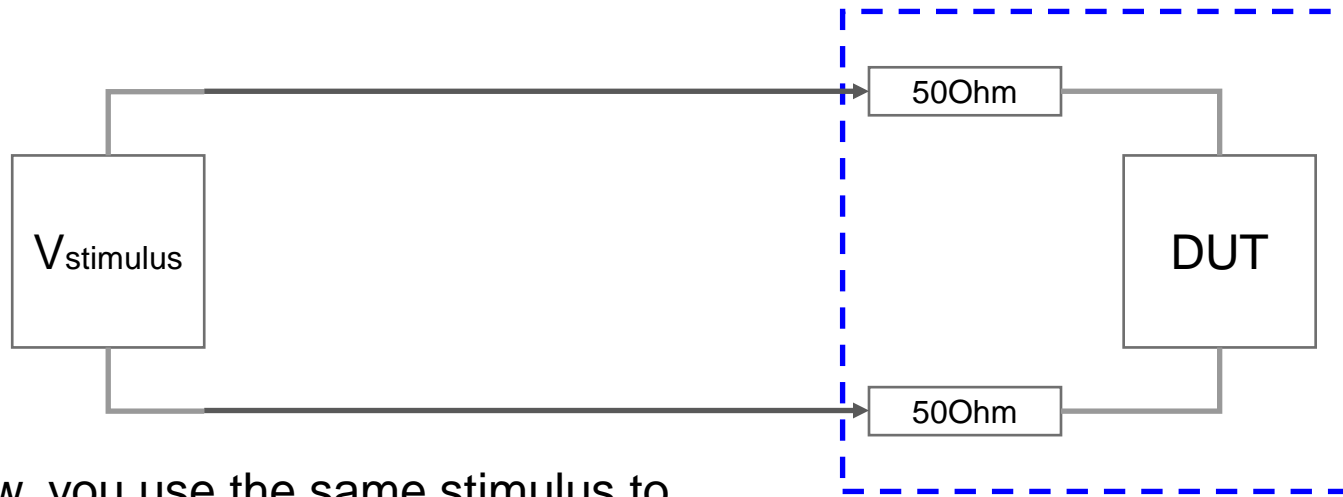

Now, you use the same stimulus to characterize the circuit inside the Blue Dashed Box, that is:

1. The same voltage swing
2. Fast rising time – 1e-21sec (1e-9ps)
3. Small time steps, no more than 1ps

Treat as an **“Whole Equalizer”**



Modeling
in **AMI**

Which we use to characterize the channel.

Characterizing - Normalizing:

```
( RX_HyperCore
  ( CTE
    ( csvfilt
      ( file D:\Case_CDNS_20160616_IBIS_AMI\Modelize_RX\CTLE_TRAN_0.5
      ( sel 0 )
      ( input 0.57 )
    )
    ( module_off 0 )
    ( csvid_file csvid.txt )
    ( td_filter_out cte_td_out.txt )
    ( adapt_cte_sel_file cte_out.txt )
  )
)
```

```
24 .subckt TX_50OUT pos neg pwr in ngnd
25
26 E1 pos ngnd volt='0.47+0.57*v(in,ngnd)'
27 E2 neg ngnd volt='1.04-0.57*v(in,ngnd)'
28
29 .ends
```

Normalize to the voltage swing you use to characterize the channel and the equalizer.


Characterizing – Normalizing (Cont'd):

Beware!!:

```
( RX_HyperCore
  ( CTE
    ( csvfilt
      ( file D:\Case_CDNS_20160616_IBIS_AMI\Modelize_RX\CTLE_TRAN_0.5
      ( sel 0 )
      ( input 0.57 )
    )
    ( module_off 0 )
    ( csvid_file csvid.txt )
    ( td_filter_out cte td_out.txt )
    ( adapt_cte_sel_file cte_out.txt )
  )
)
```

```
24 .subckt TX_50OUT pos neg pwr in ngnd
25
26 E1 pos ngnd volt='0.47+0.57*v(in,ngnd)'
27 E2 neg ngnd volt='1.04-0.57*v(in,ngnd)'
28
29 .ends
```

 
You may wonder the input stimulus is $2 \times 0.57 = 1.14\text{V}$,



Why do we
normalize it
to **0.57v**?

Characterizing – Normalizing (Cont'd):

The answer is:

 



HERE!!

Question: What if you are using an IBIS model which is equivalent to a 90Ω terminator instead of a 100Ω ?

Correlation – Channel Analysis

between the IBIS-AMI and the Transistor Netlist

Under a simple test environment:

 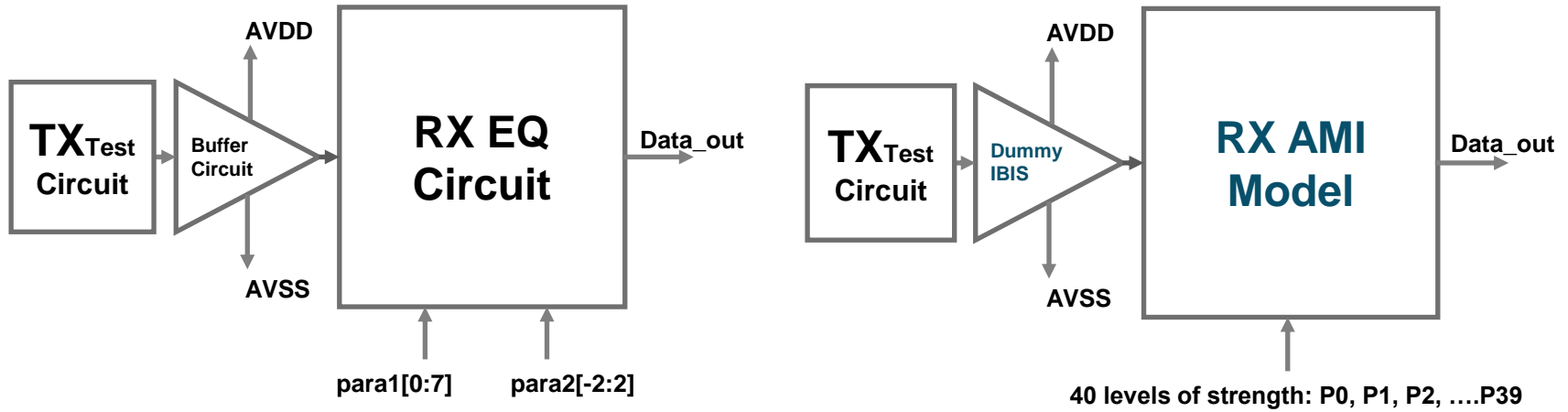


Red: Eye Contour of Transistor Netlist under Channel Analysis


Blue: Eye Contour of IBIS-AMI model under Channel Analysis

Correlation – Mid Length Channel


Transient Analysis:

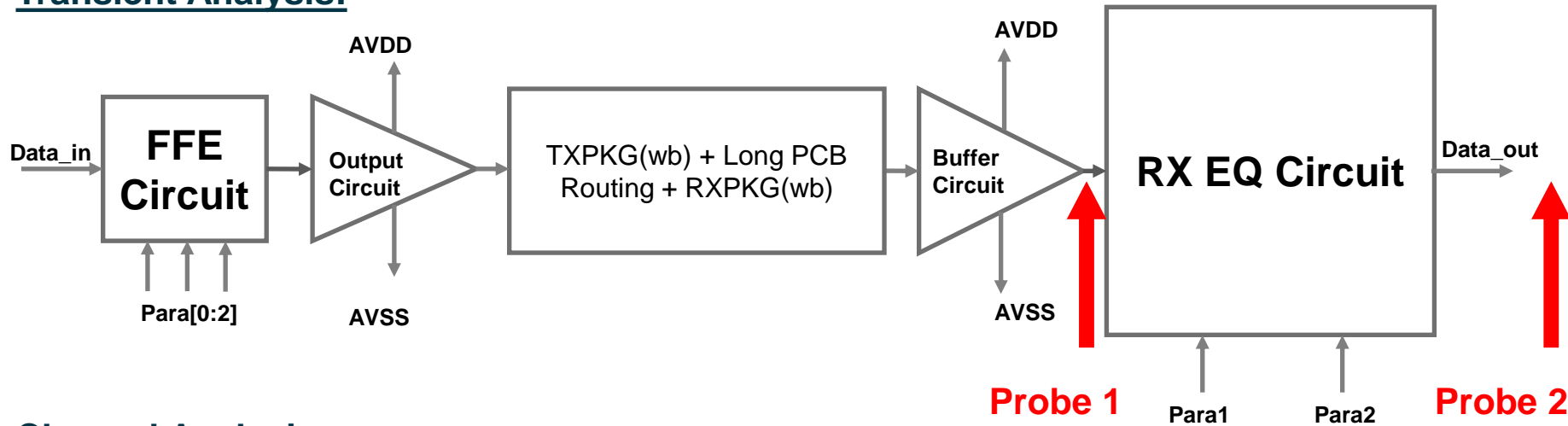


Channel Analysis:

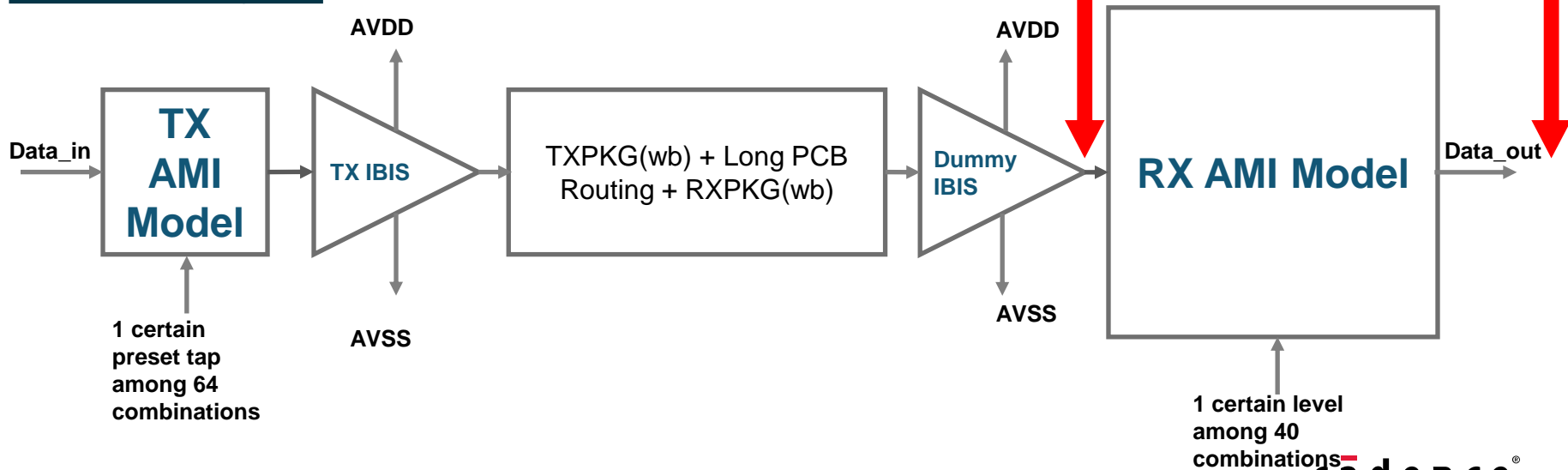

 Correlation – Mid Length Channel (**Probe 1**)




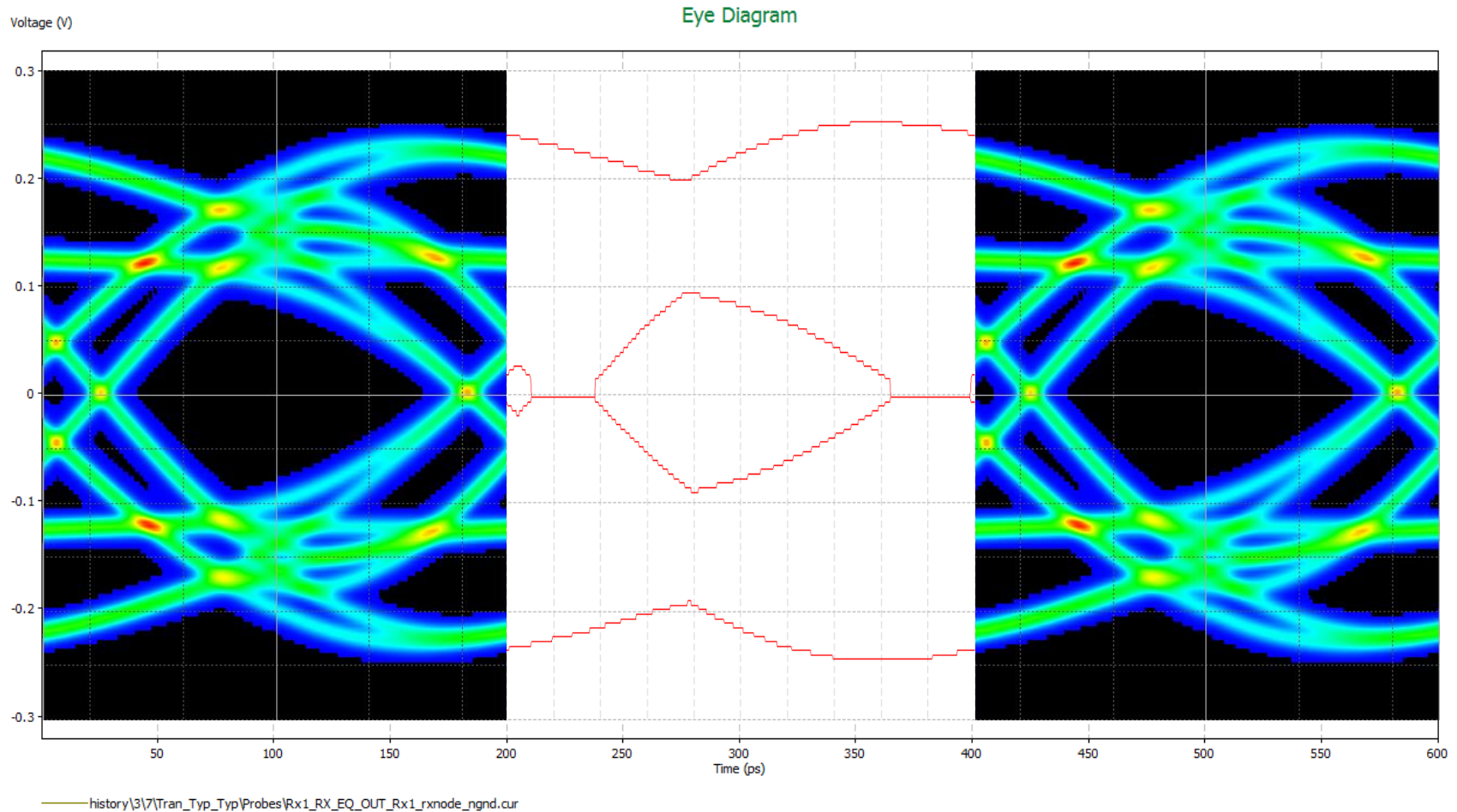Correlation – Mid Length Channel (**Probe 2**)




Correlation – Long Length Channel


Transient Analysis:

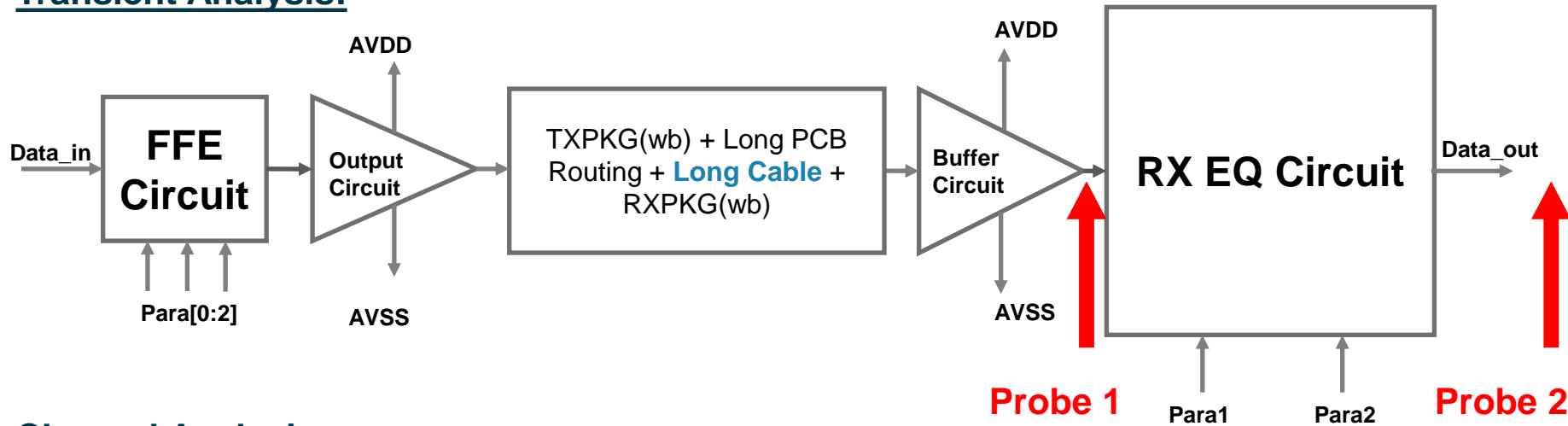


Channel Analysis:

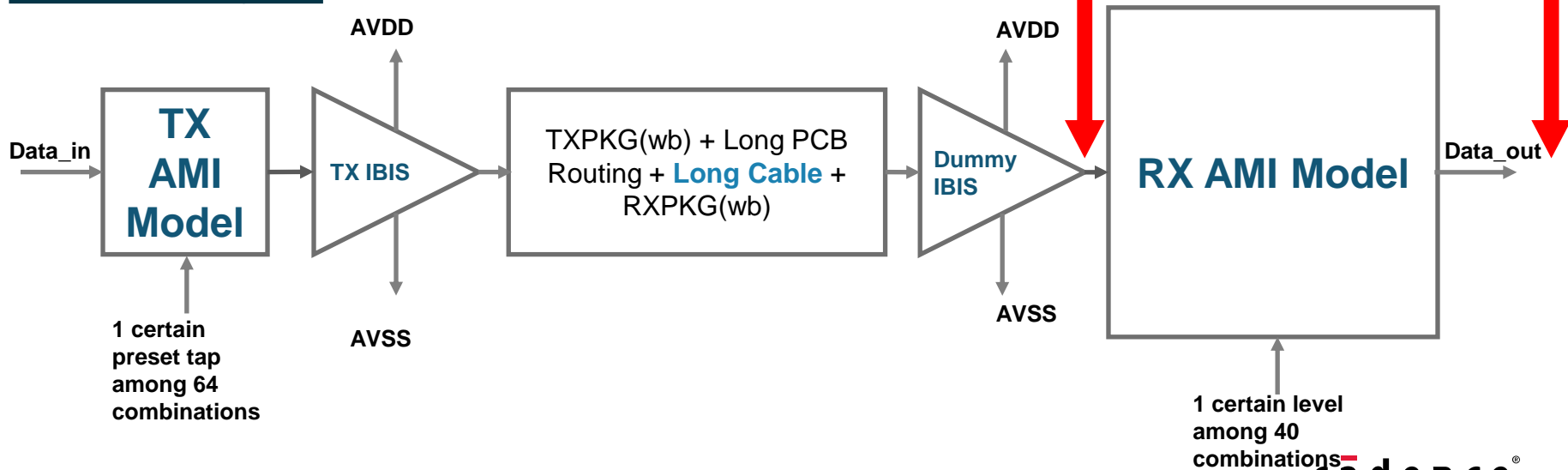

 Correlation – Long Length Channel (**Probe 1**)



 
Correlation – Long Length Channel (**Probe 2**)



Limitation


This method is only valid while being applied to a pure CTLE which is composed of linear components, such as R, L, C, Linear E(VCVS), Linear F(CCCS)...etc.

Or in short, a CTLE which satisfies:

 

Limitation (Cont'd)

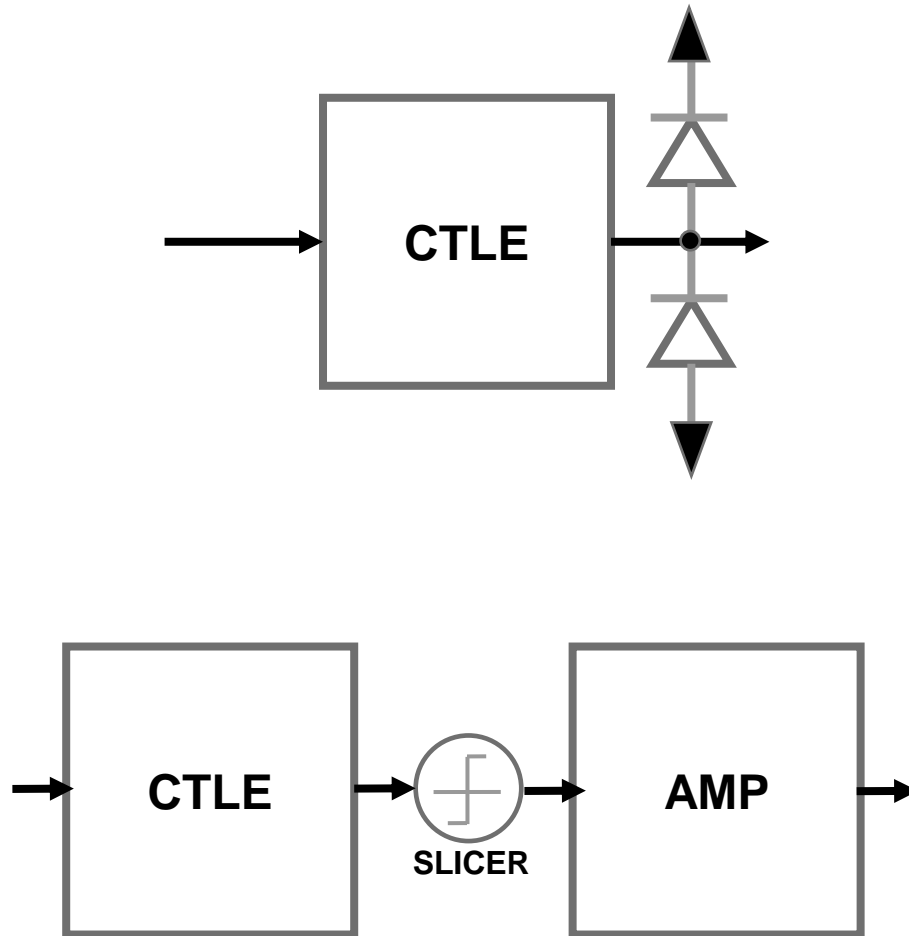There're still lots of circuits not suitable for this method. For example:




Conclusion


- Cutting/Dividing the whole design is a necessary process during RX IBIS-AMI modeling. This slides provides a method which guarantees the combination of the sub-designs so-divided is exactly equivalent to the original whole design.
- Also, the method in this slides benefits modelers that they will no longer need to model a RX IBIS model. A dummy IBIS will be used for all cases while the buffer characteristics has been modeled into the AMI model. No cutting/dividing is needed any more.
- This slides provides a method to generate IBIS-AMI simply by characterizing the V/T of the netlist – away more accurate than generating IBIS-AMI by inputting parameters values.
- However, this method is only valid while being applied to a purely linear equalizer, that is, there exists a purely linear relationship between the input and output of the equalizer.
- What else? Can a TX FFE be modeled simply by characterizing? Can an non-linear RX CTE be modeled simply by characterizing?

Correlation – Mid Length Channel


In fact, now we've even developed a flow which can successfully model a **non-linear DFE-free** RX EQ with very good accuracy simply by characterizing: **Example 1**

 

Probe 1

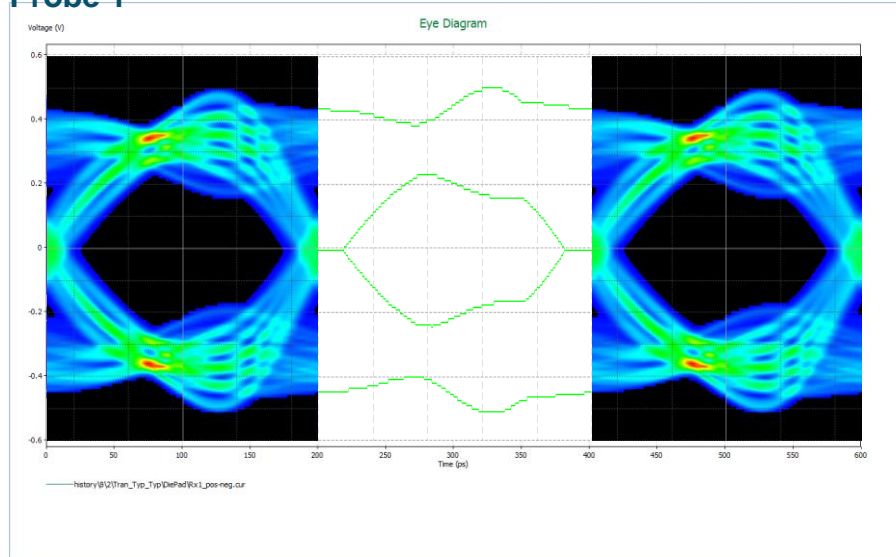


Probe 2

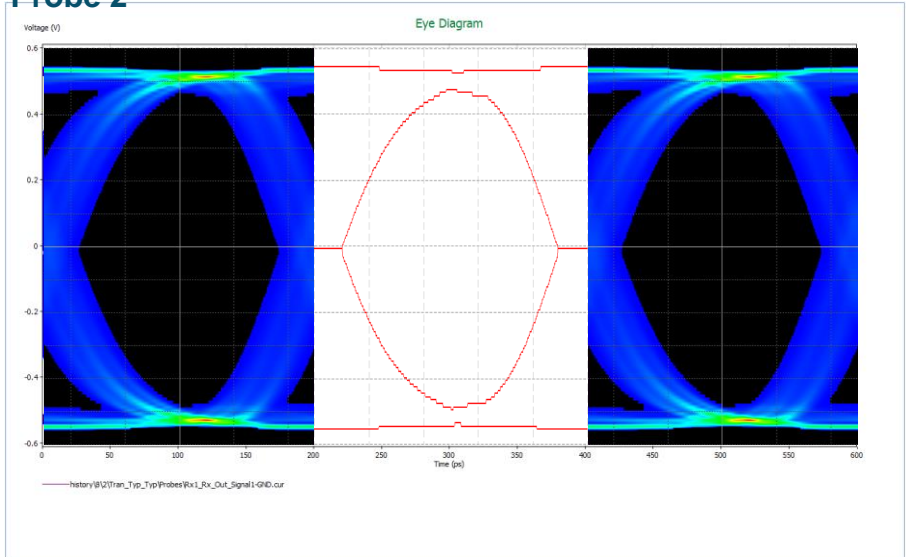


Correlation – Long Length Channel


In fact, now we've even developed a flow which can successfully model a **non-linear DFE-free** RX EQ with very good accuracy simply by characterizing: **Example 2**

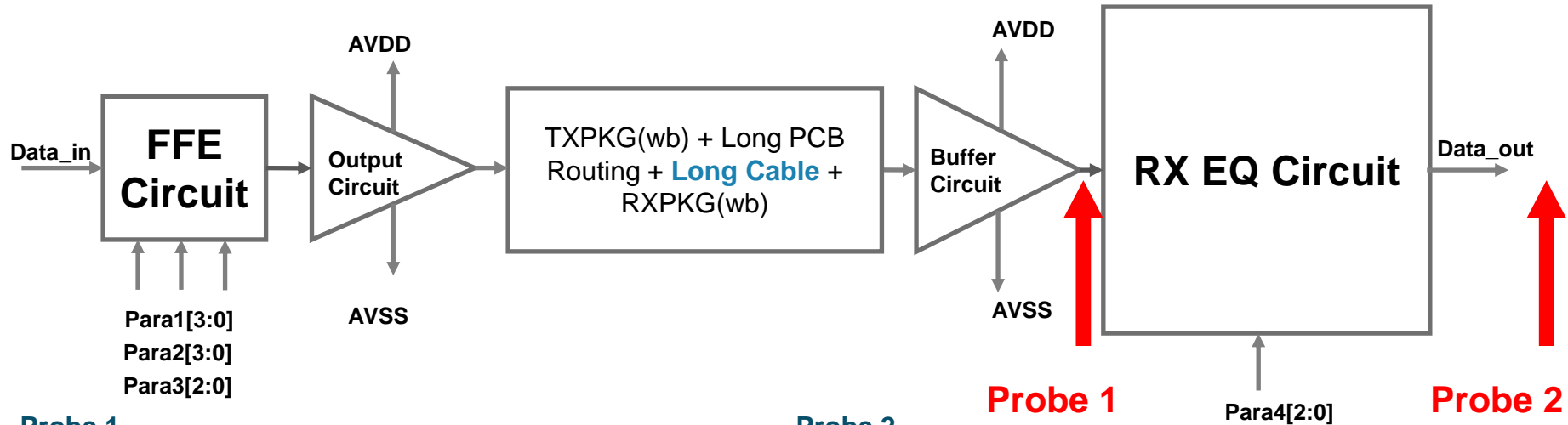

Probe 1

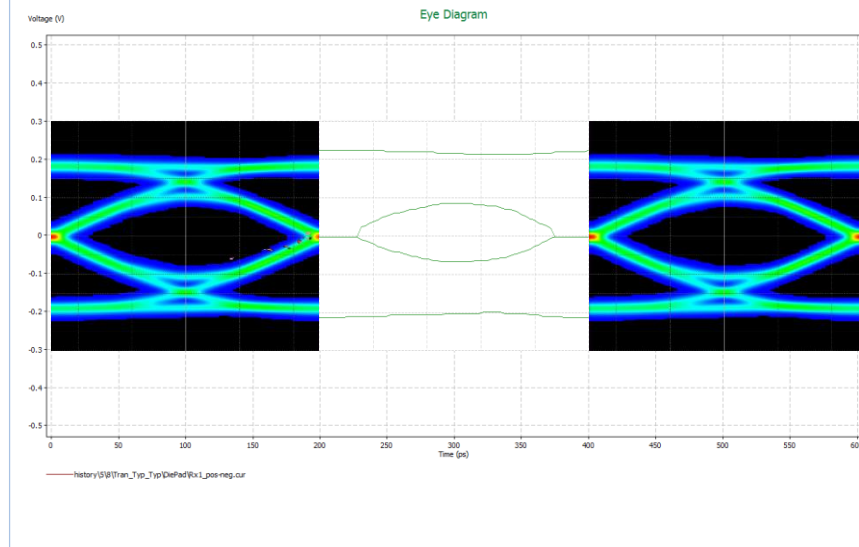

Probe 2

 

See you on IBIS Summit 2018

cā dence®

© 2017 Cadence Design Systems, Inc. All rights reserved worldwide. Cadence, the Cadence logo and Spectre are registered trademarks and Sigrity, SystemSI, and T2B are trademarks of Cadence Design Systems, Inc. in the United States and other countries.. All rights reserved. All other trademarks are the property of their respective owners.