




Multi-Element C_comp Modeling

*Michael Mirmak
Intel Corporation*

*IBIS Summit
PCB East 2004
October 4, 2004*

09/27/04
*Other brands and names are the property of their respective owners

Page 1


Agenda

- **Background**
 - Recall C_comp “Back Out” Experiments
 - Transient Matching
 - AC Differential- and Common-mode Behaviors
- **Creating a Better AC Model for C_comp**
 - Simulation Data in AC Domain
 - The Giacotto-Muranyi Model
 - Improvements on the G-M Model
 - Analytic vs. EDA Tool Solutions
 - Results
 - Applying G-M Models to the Differential Case
 - Next Steps

Note: many slides in this presentation are animated

09/27/04
*Other brands and names are the property of their respective owners


Page 2



from April '04 Summit

How is C_comp data collected?

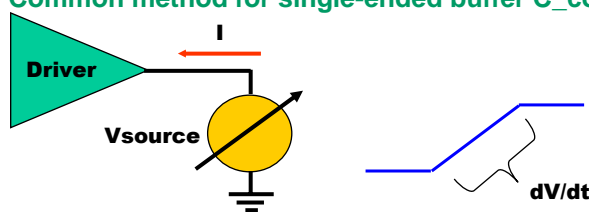- Common method for single-ended buffer C_comp



1. Use Vsource with known edge rate, dV/dt
2. Measure the input current
3. Calculate capacitance (may have to take an average)

$$I = C * \frac{dV}{dt} \quad \rightarrow \quad C = \frac{I}{\left(\frac{dV}{dt}\right)}$$

What about for the differential case?
How about pre-emphasis (wired-or structures)?


09/27/04
*Other brands and names are the property of their respective owners

Page 3

Desktop Platforms GROUP

from April '04 Summit

IBIS for SerDes Pre-Emphasis

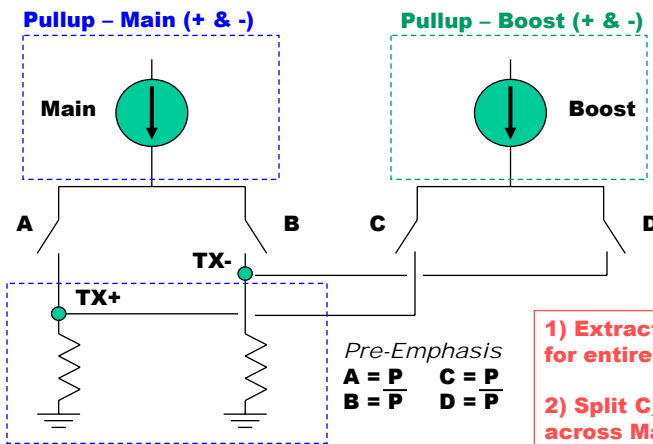

Pullup – Main (+ & -)

Main

Pullup – Boost (+ & -)

Boost

A

B

C

D

TX+

TX-

Ground Clamps

Main + & -

Pre-Emphasis

$A = P$ $C = P$

$B = P$ $D = P$

De-Emphasis

$A = P$ $C = P$

$B = P$ $D = P$



1) Extract C_comp for entire buffer



2) Split C_comp across Main, Boost

09/27/04
*Other brands and names are the property of their respective owners

Page 4

Desktop Platforms GROUP

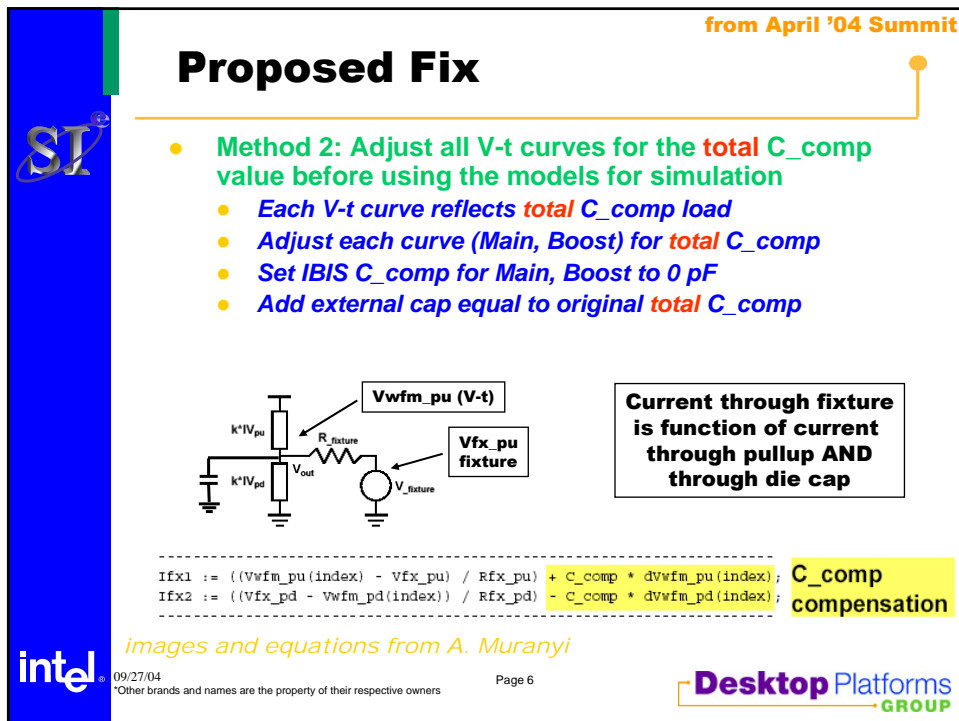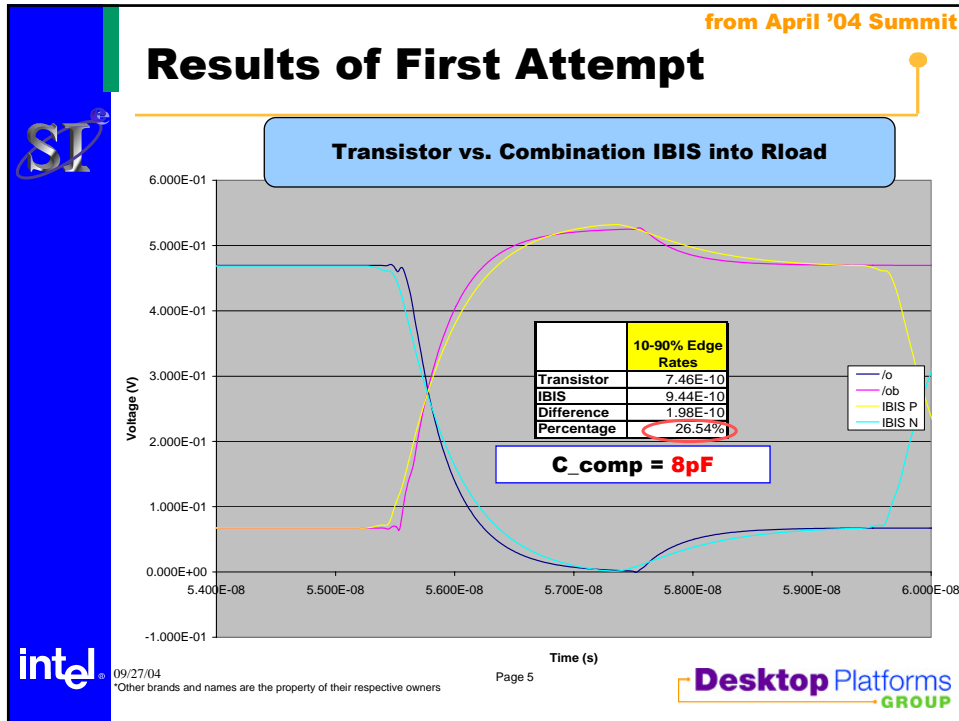


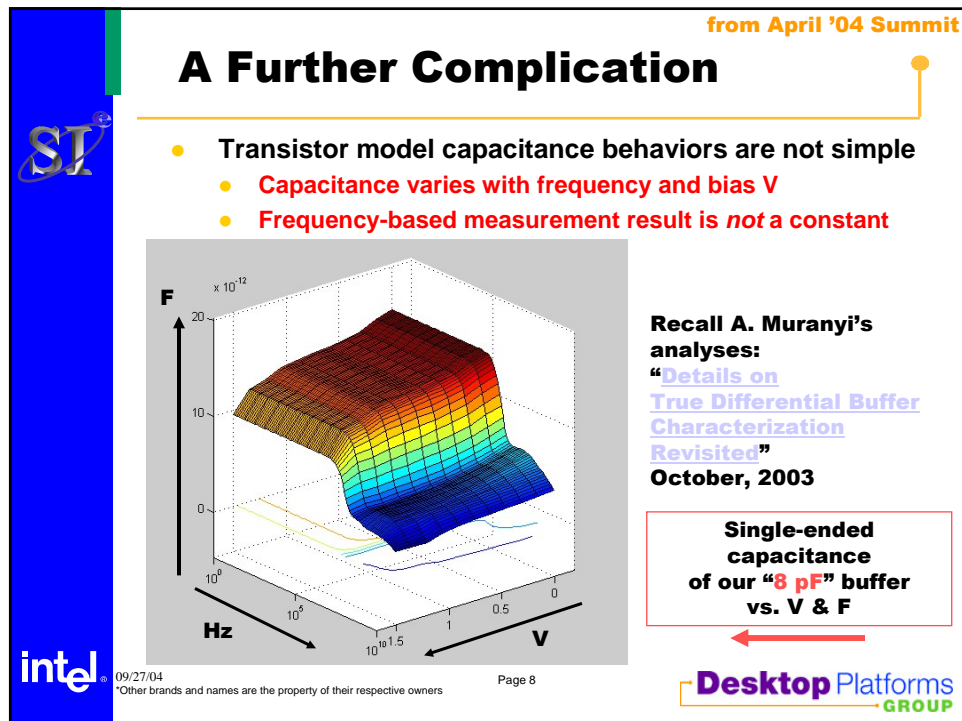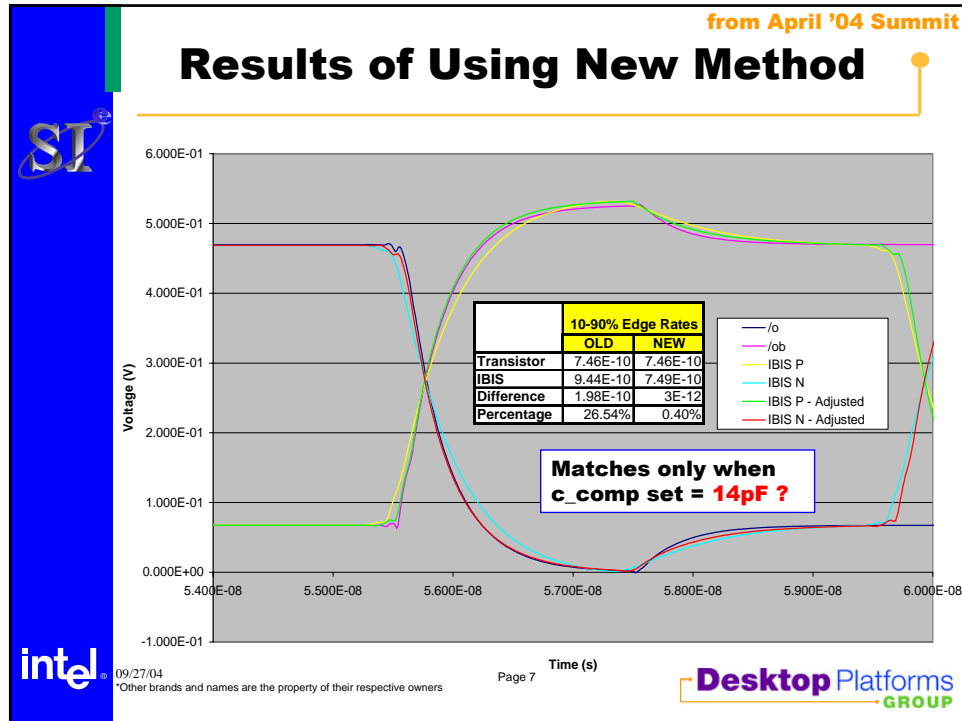

from April '04 Summit

A Further Complication

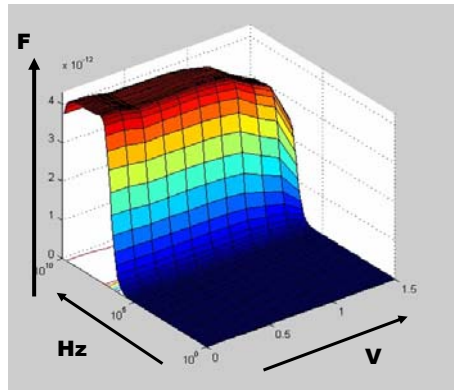- Differential view of transistor model capacitance
 - Differential capacitance not included in adjusted model
 - Note that finding of femto-farad differential capacitances described in previous summits may not always apply!



Recall A. Muranyi's analyses:

[“Details on True Differential Buffer Characterization Revisited”](#)

October, 2003

Differential capacitance of our “8 pF” buffer vs. V & F



Desktop Platforms GROUP

intel

09/27/04

*Other brands and names are the property of their respective owners

Page 9

Another New Approach

- First C_comp adjustment attempt made two assumptions
 - Differential buffers can be “split” in two
 - Each can be modeled adequately with a single C_comp
- Additional data calls at least one assumption into question
 - Single C_comp does not permit frequency dependence
 - A differential component appears at some frequencies
- Proposal: Stay in AC Domain for C_comp Measurement
 - Attempt to match AC behavior of simulation model
 - Once model correlates in frequency of interest, add data into IBIS model
 - This may stretch IBIS 3.2/4.0 beyond available keywords



intel



09/27/04



*Other brands and names are the property of their respective owners

Page 10

Desktop Platforms GROUP

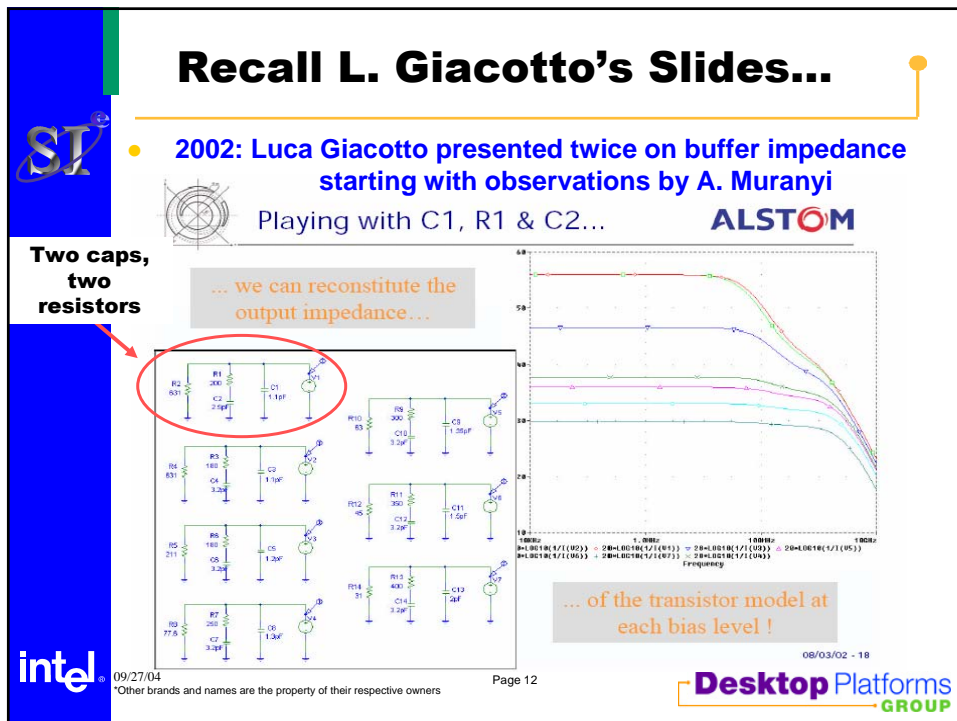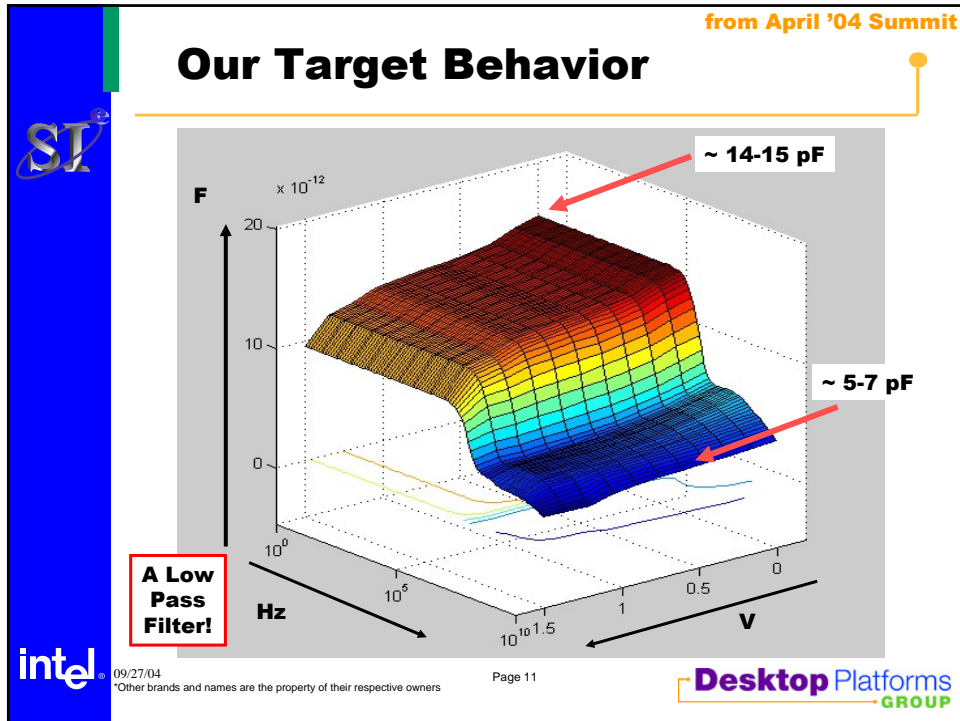


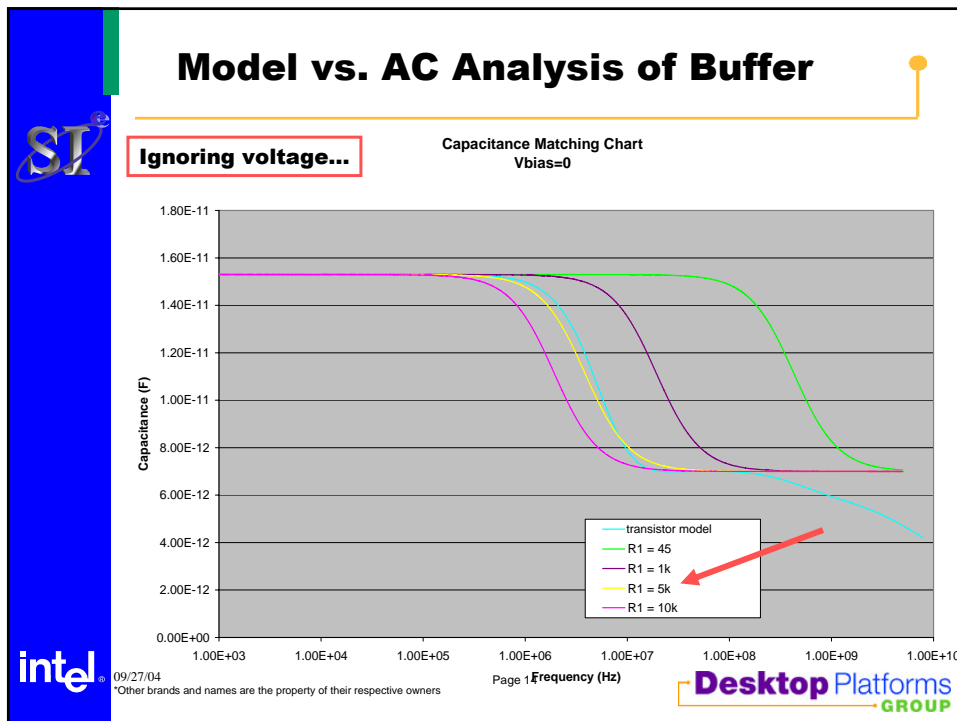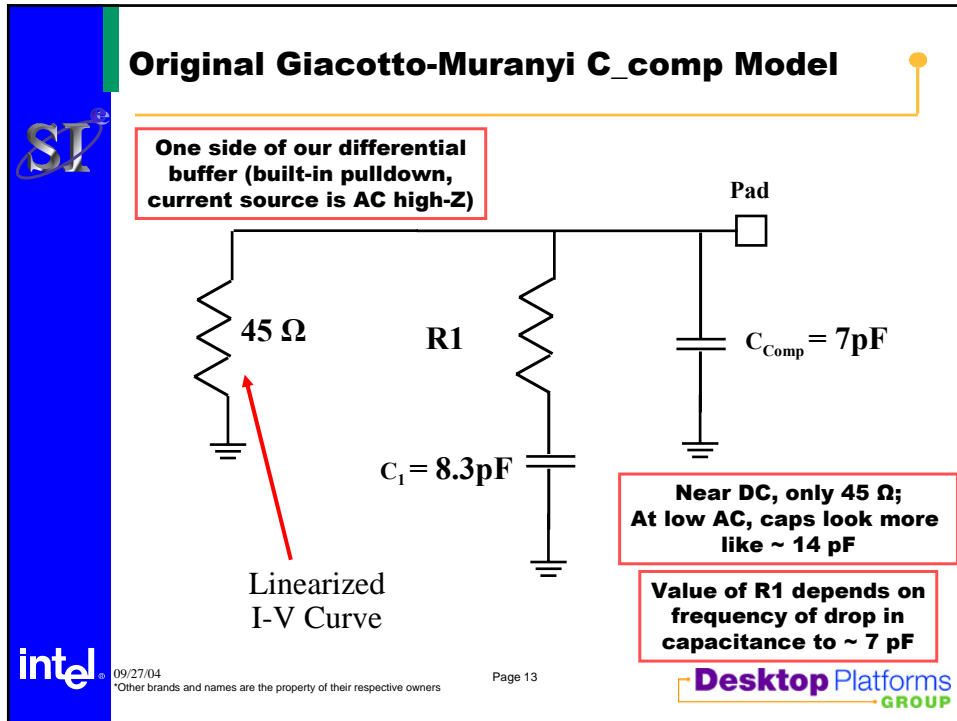

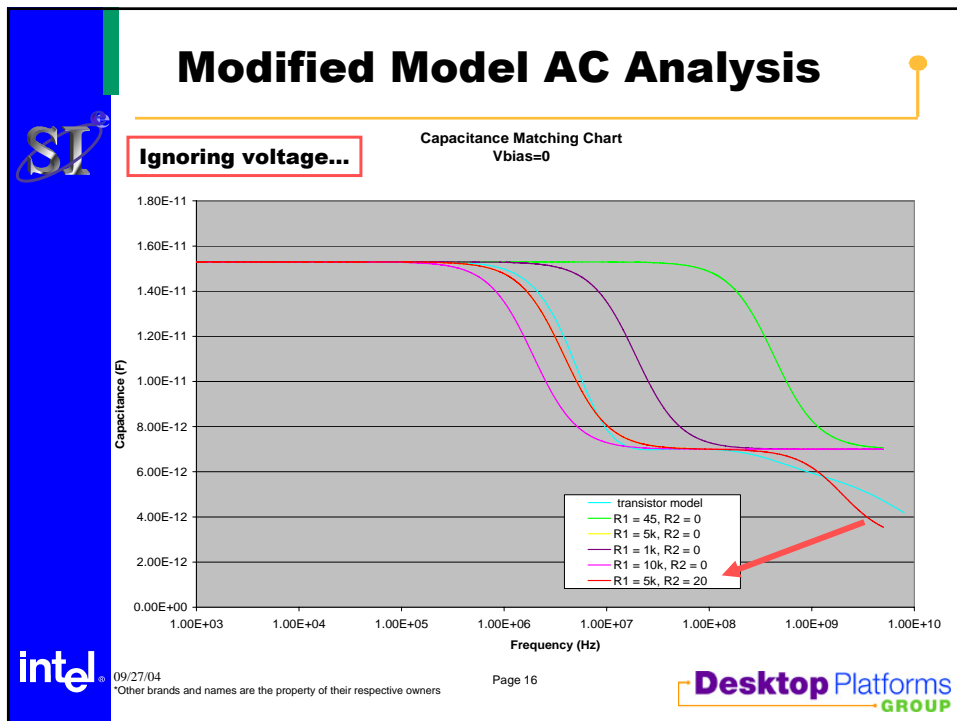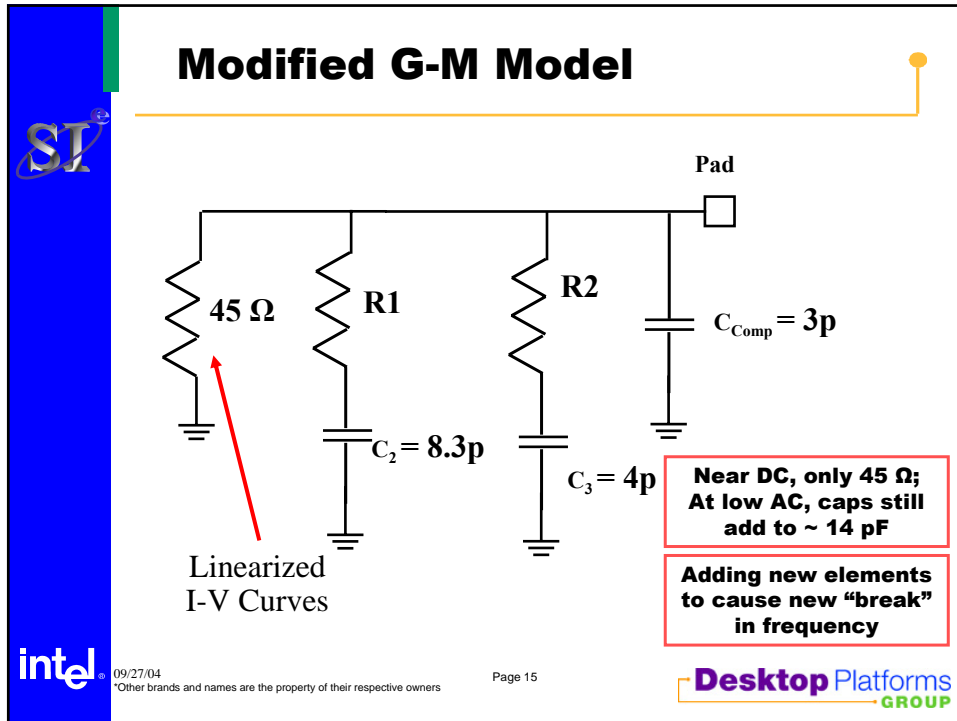

Model Assessment

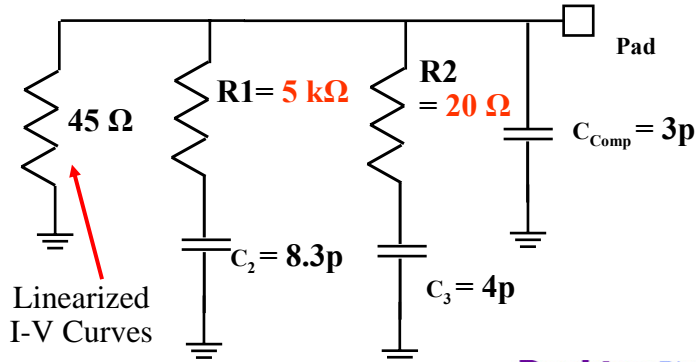- Model is a fair match up to ~ 2 GHz
- Problems arise
 - A single C_{comp} value is no longer adequate
 - No IBIS keywords support this structure
 - Still need to "back out" these elements from V-t curves



intel


09/27/04
*Other brands and names are the property of their respective owners

Page 17

Desktop Platforms
GROUP

Original C_{comp} Adjustment

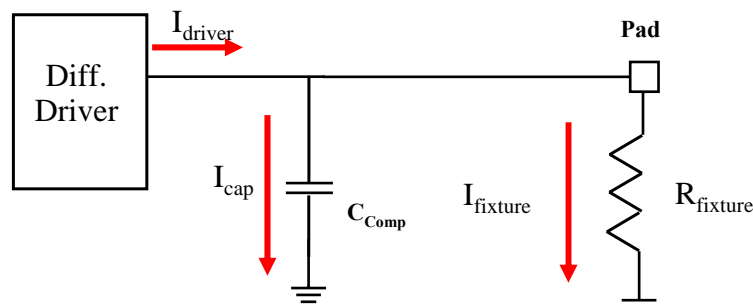- $I_{driver}(t) = I_{cap}(t) + I_{fixture}(t)$
- $I_{cap} = C_{comp} * dV/dt$ where dV/dt is instantaneous V-t slope
- $I_{fixture} = V-t/R_{fixture}$, taken at every time point
- "Cap-less" V-t curve = $I_{driver}(t) * R_{fixture}$
 - Driver is pullup curve set with internal pulldowns
 - $V_{fixture} = 0$, since there is no active, driving pulldown



intel

09/27/04
*Other brands and names are the property of their respective owners


Page 18

Desktop Platforms
GROUP

Modified Approach

- $I_{\text{driver}}(t) = I_{\text{cap}}(t) + I_{\text{fixture}}(t) + I_1 + I_2$
- $I_{\text{cap}} = C_{\text{comp}} * dV/dt$ where dV/dt is instant. slope of V-t
- $I_{\text{fixture}} = V-t/R_{\text{fixture}}$, taken at every time point
- "Cap-less" V-t curve = $I_{\text{driver}}(t) * R_{\text{fixture}}$
- $I_1(t) = C_1 * dV_1/dt$
- $I_1(t) = \{V-t - V_1(t)\}/R_1$
- $I_2(t) = C_2 * dV_2/dt$
- $I_2(t) = \{V-t - V_2(t)\}/R_1$

But
we don't know V or I!!!

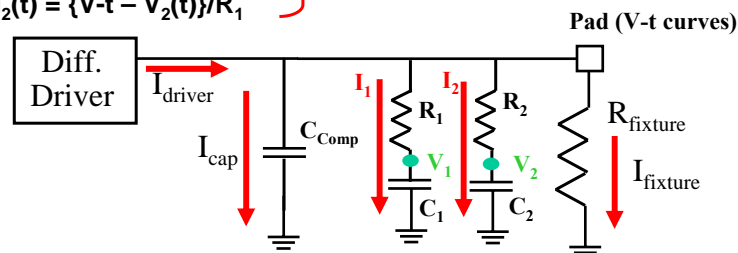

intel

09/27/04
*Other brands and names are the property of their respective owners

Page 19


Desktop Platforms
GROUP

Modified Approach (2)

- Yes, we do know...
- RC charge equation is $V_1 = V_i + Ae^{-t/RC}$
 - see Horowitz and Hill, *The Art of Electronics*, Chapter 1
- For arbitrary $V_i(t)$, this becomes

$$V(t) = \frac{1}{RC} \int_{-\infty}^t V_i(\tau) e^{-(t-\tau)/RC} d\tau$$

- If $I_1(t) = C_1 * dV_1/dt...$

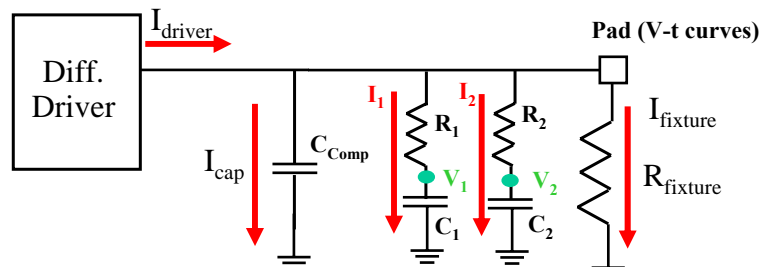

intel


09/27/04
*Other brands and names are the property of their respective owners

Page 20

Desktop Platforms
GROUP

Modified Approach (3)

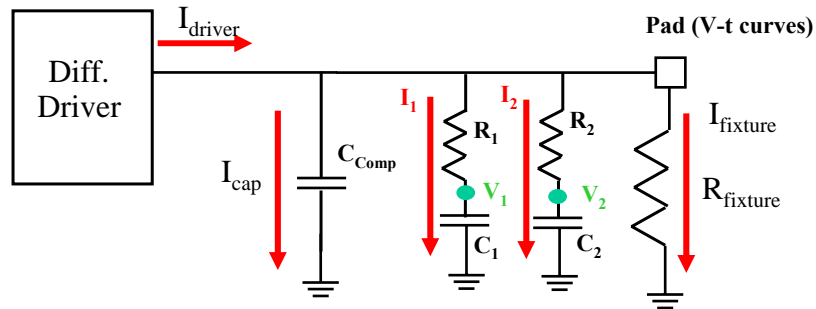- Very tricky differential equation...
- Easier solution – use EDA tool to generate data!
 - Create netlist as shown
 - Drive PWL source with original V-t data set(s), at pad
 - CCCS into load = R_{fixture} provides “adjusted” V-t curves



intel

09/27/04
*Other brands and names are the property of their respective owners


Page 21

Desktop Platforms
GROUP

New “Cap-less” Main V-t Table

Adjusted “Cap-less” V-t curve

Rising Only


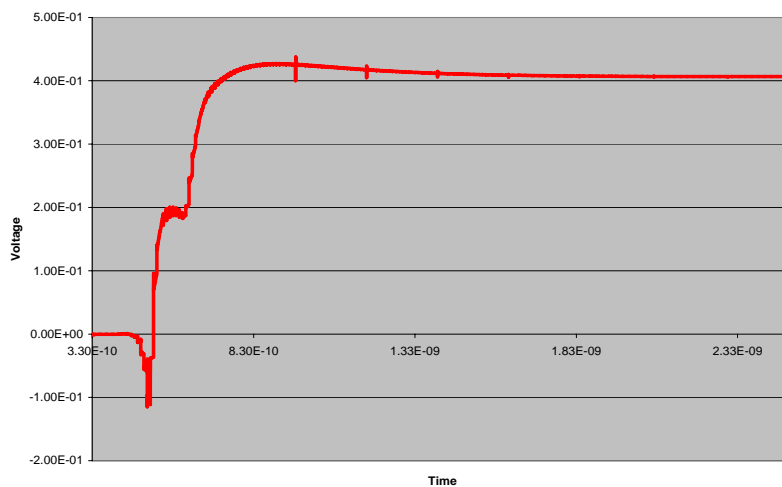




intel



09/27/04
*Other brands and names are the property of their respective owners



Page 22


Desktop Platforms
GROUP

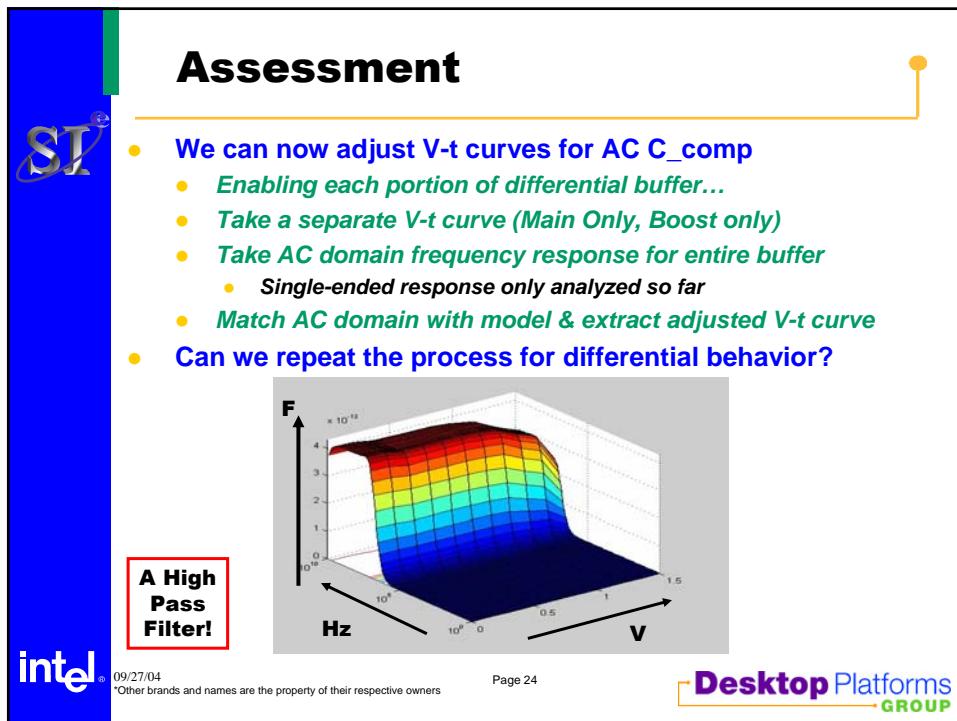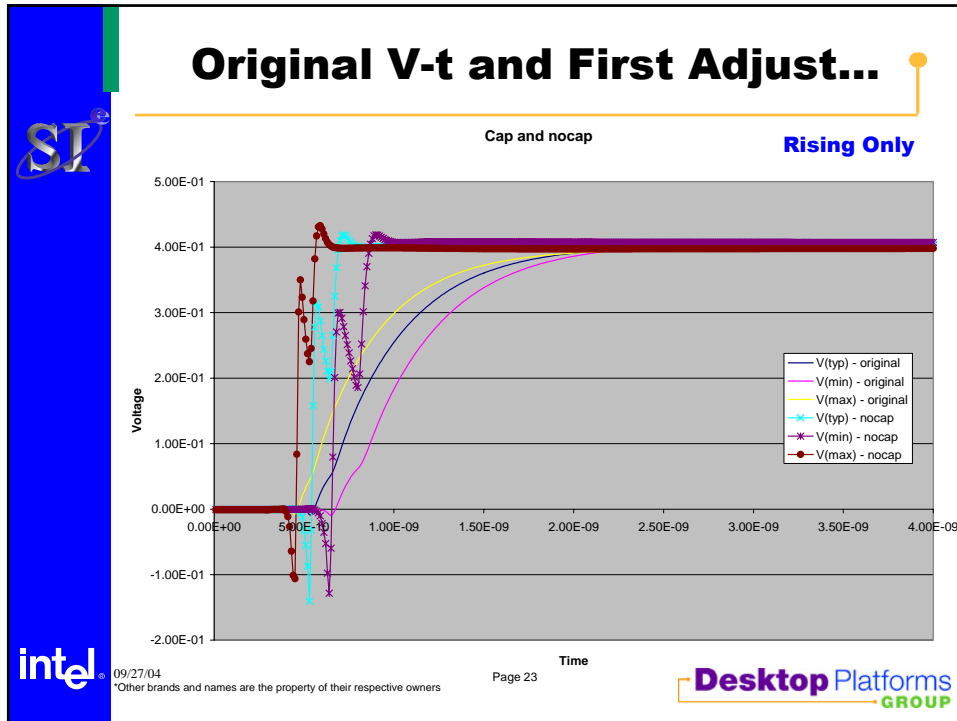

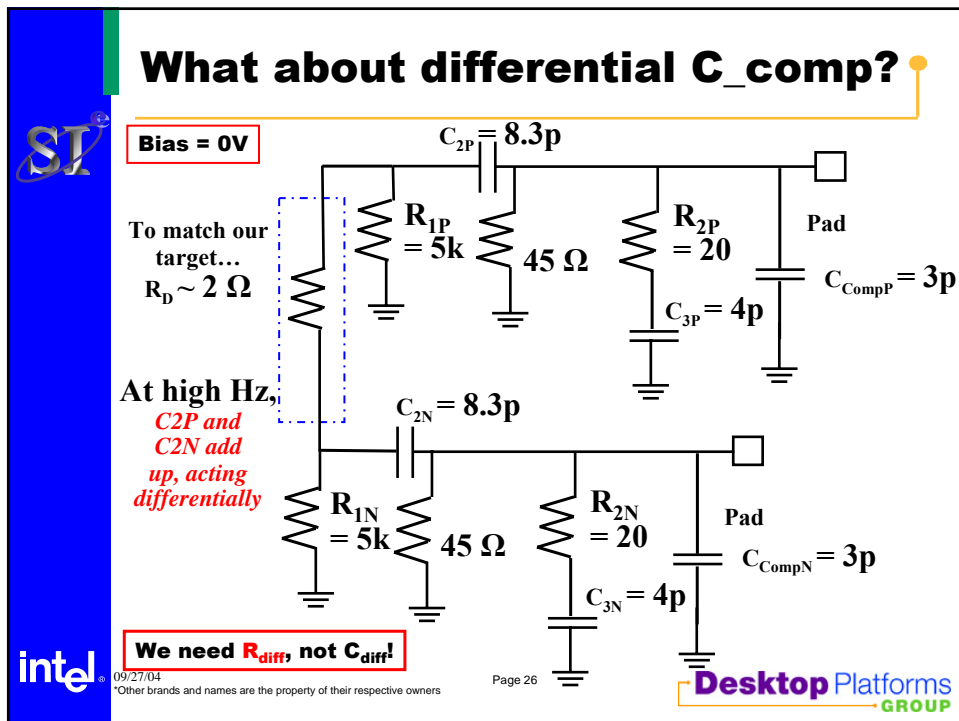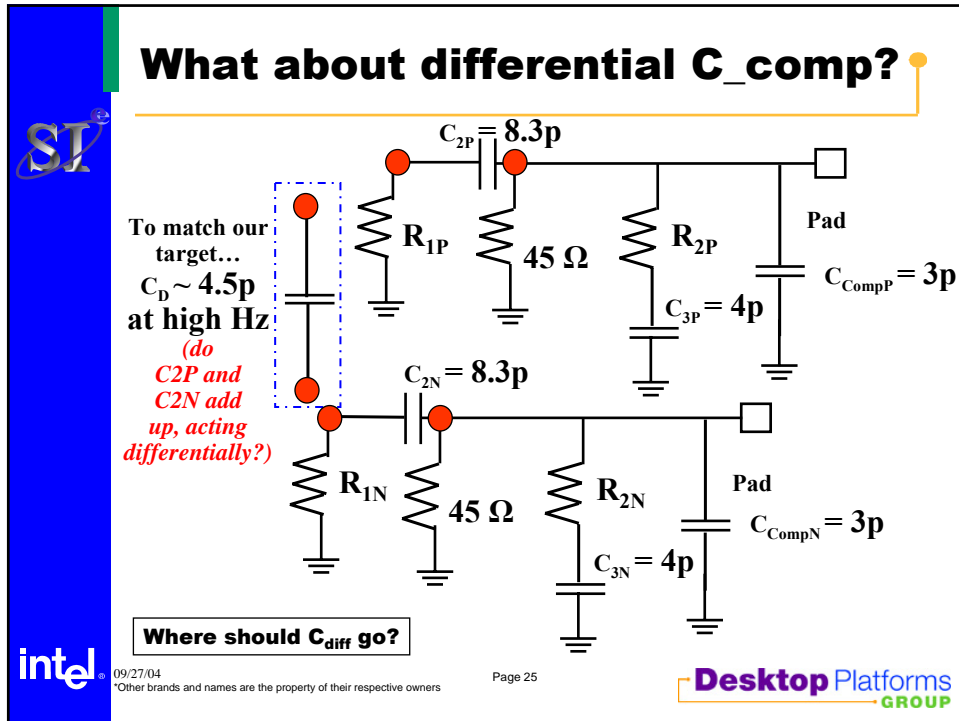

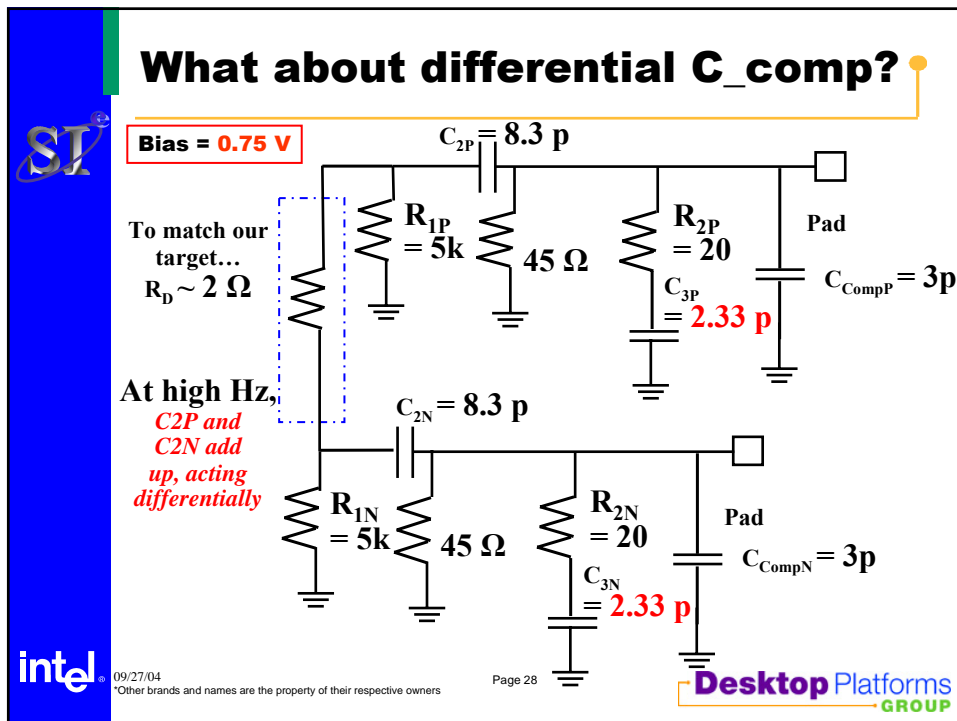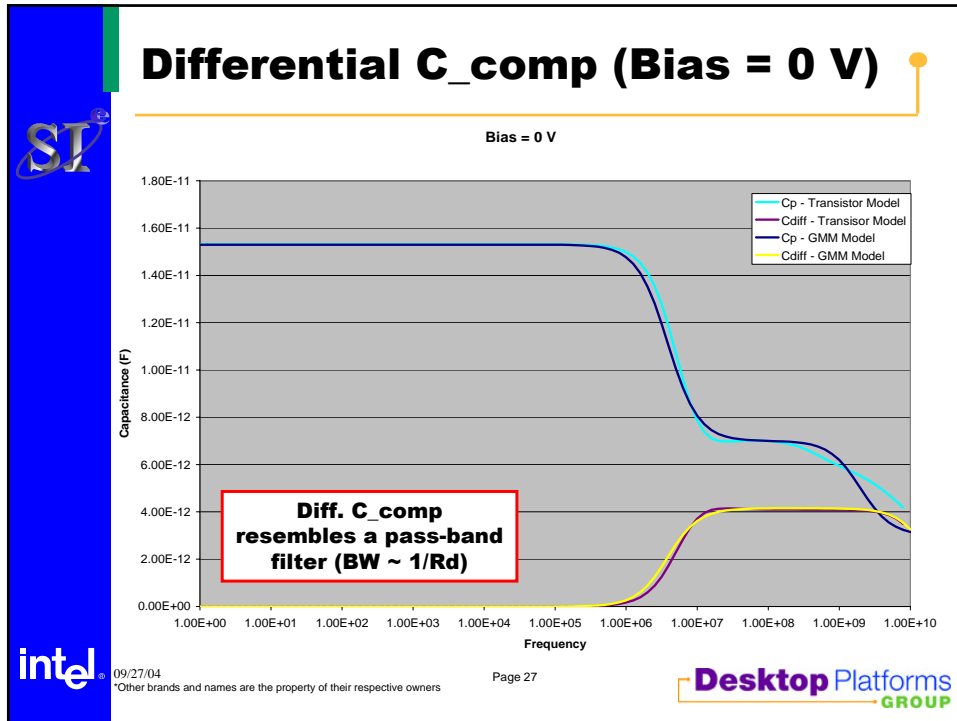

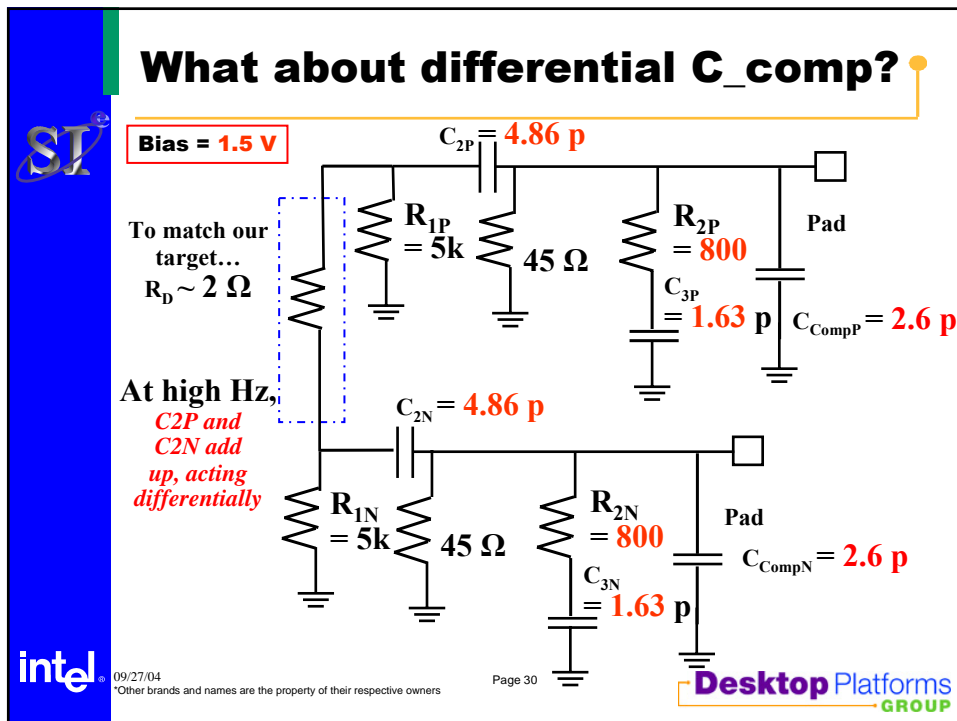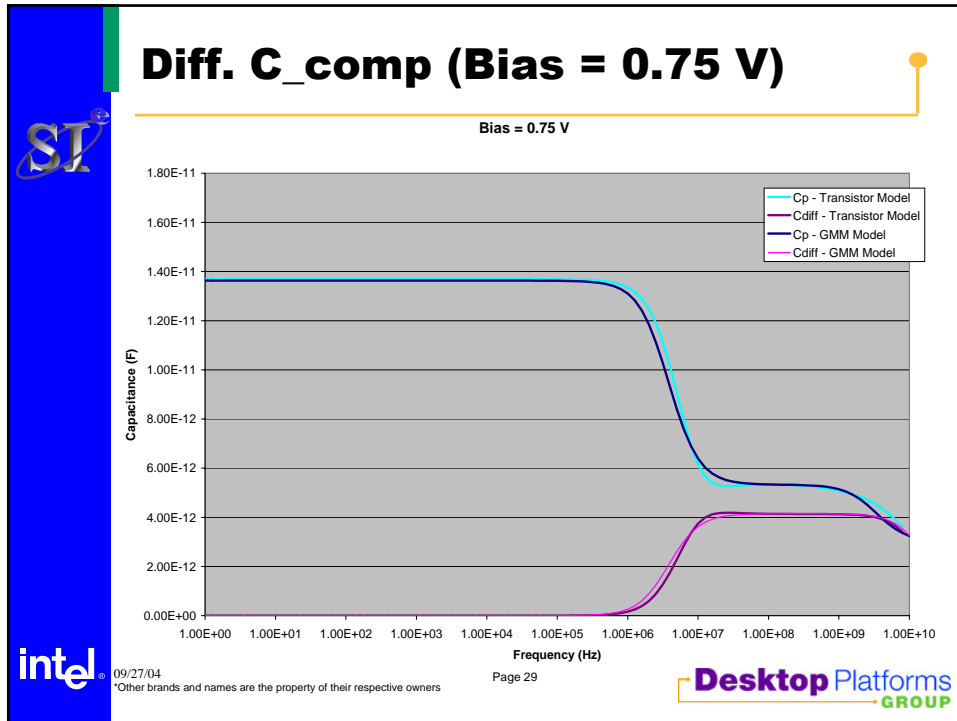

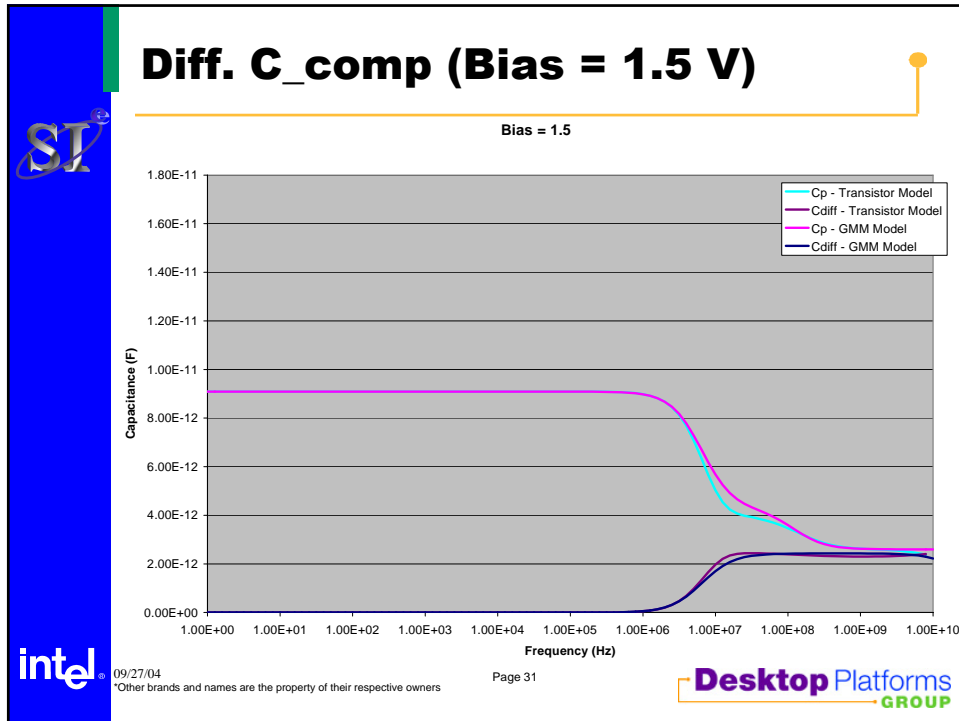

Summary and Next Steps

- **A new method for adjusting V-t curves is shown**
 - *Based on frequency-domain capacitance profile*
 - *Fit to a circuit expanded from Giacotto-Muranyi model*
 - *Covers both differential and single-ended AC behavior*
- **Comments and Next Steps**
 - *Method is untested in system simulation!*
 - EDA tool method (CCCS) does not generate clean V-t data
 - Local IBIS creation tools will choke on “noise” in V-t data
 - *Need analytic method of model value fit*
 - Values here determined using trial-and-error; fit isn't great
 - Giacotto proposed pole-zero analysis
 - No luck in getting PZ to generate matching RC values
 - Will all models have the same RC model profile?
 - *Need to incorporate more voltage bias data*
 - *Need a recommendation for model bandwidth*

09/27/04
*Other brands and names are the property of their respective owners

Page 32

Desktop Platforms GROUP

BACKUP

09/27/04
*Other brands and names are the property of their respective owners

Page 33

